

SMJE 3173

Digital System

Week 5: Arithmetic Circuits Part 1

- Binary Number Representation

- ☐ Sign & Magnitude
- ☐ Ones Complement
- ☐ Twos Complement

- Networks for Binary Addition

- ☐ Half Adder
- ☐ Full Adder
- ☐ Ripple Adder
- ☐ Subtractor



Motivation

- Arithmetic circuits are excellent examples of combinational logic design

- Time vs. Space Trade-offs
 - Doing things fast requires more logic and thus more space
 - Example: carry look ahead logic

- Arithmetic Logic Units
 - Critical component of processor datapath



Unsigned Integers

- Only positive numbers are called **unsigned** numbers
- Smallest representable value: bit
- Bit groups represent information –
 - 4 bits in a group : nibble
 - 8 bits in a group : byte
 - 2^{10} in a group : kilo e.g. kilo, kilobytes (kB)
- Number of bits determine max. combinations of information -

N bits = 2^N values

Number of Bits	Number of values	Machine
4	16	Intel 4004
8	256	8080, 6800
16	65536	PDP11, 8086, 68000
32	$\sim 4 \times 10^9$	IBM 370, 68020, VAX11/780, IEEE single
48	1×10^{14}	Unisys
64	1.8×10^{19}	Cray, IEEE double



Unsigned Integers

- Value for the bit pattern:

$$V_{unsigned} = \sum_{i=0}^{N-1} b_i \times 2^i$$

$$V = b_0 \times 2^0 + b_1 \times 2^1 + b_2 \times 2^2 + \dots b_{N-1} \times 2^{N-1}$$

- Example:

$$10110_2 = 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 = 22_{10}$$

- How many numbers can 8-bit represent?
- For N bits, range of values:
0 up to $2^N - 1$



Representation of Negative Numbers

- Representation of positive numbers are the same in most systems
- Major differences are in how negative numbers are represented. There are 3 major schemes:
 - sign and magnitude
 - ones complement
 - twos complement
- Assumptions:
 - 4-bit machine word
 - 16 different values can be represented
 - 7, -6, -5, -4, -3, -2, -1, 0, 1, 2, 3, 4, 5, 6, 7, 8
 - roughly half are positive, half are negative




Sign and Magnitude (SAM)

- Easiest to understand
- Method:
 - (i) Leftmost bit (MSB) is sign bit
 - 0 means positive e.g. $+18 = 00010010$
 - 1 means negative e.g.
 - (ii) Represent the magnitude of the number in true binary form
- Example:
 - $+18 = 00010010$
 - $-18 = 10010010$



Sign and Magnitude

 

Summary : (Example for 4-bit number representation; N= 4)

- High order bit is sign: 0 = positive (or zero), 1 = negative
- Three low order bits is the magnitude: 0 (000) thru 7 (111)
- Number range for n bits = $\pm(2^{n-1}-1)$
- Two representations for 0 (0000 and 1000)



Sign-and-Magnitude Problems

- Easy for humans to understand, but may not be the best for machine operation efficiency
- Cumbersome addition/subtraction
- Must compare magnitudes to determine sign of result
- Need to check both sign and magnitude in arithmetic
- Two representations of zero (+0 and -0)



Ones' Complement Representation

- Ones' complement defined algebraically as

$$\overline{N} = (2^n - 1) - N$$

- For example:

(i) Find 2's complement of 5 (i.e. -5) in 4-bit representation

$$N = (2^4 - 1) - 5$$

$$N = 1111 - 0101 = 1010_{1's} = -5$$

- Theoretically, in ones' complement we get the negation of a number by flipping (reversing) all the bits
- The name ones' complement comes from the fact that we could also get the negation of a number by subtracting each bit from 1
- Complement of a complement generates original number



Ones' Complement Representation by algebraic

$$\overline{N} = (2^n - 1) - N$$

- Ones' complement of +7
 - Since $n=4$, $(2^n - 1) = 1111$

$2^n - 1$	1	1	1	1	
N	0	1	1	1	(+7)
\overline{N}	1	0	0	0	(-7)

- Ones' complement of -7

$2^n - 1$	1	1	1	1	
N	1	0	0	0	(-7)
\overline{N}	0	1	1	1	(+7)

Shortcut method:

simply perform bitwise complement

1001 \rightarrow 0110

N	0	1	1	1	(+7)
$N_{2's}$	1	0	0	0	(-7)




Addition and Subtraction : Ones Complement

4	0100	-4	1011
<u>+ 3</u>	<u>0011</u>	<u>+ (-3)</u>	<u>1100</u>
7	0111	-7	10111
	End around carry		└─→ 1
			<u>1000</u>

4	0100	-4	1011
<u>- 3</u>	<u>1100</u>	<u>+ 3</u>	<u>0011</u>
1	10000	-1	1110
End around carry	└─→ 1		
	0001		



Ones' Complement Representation

 

Summary

- Some complexities in addition
- Subtraction implemented by addition & 1's complement
- Still two representations of 0! This causes some problems



Two's Complement

- Two's complement defined as

$$N^* = 2^n - N \text{ for } N \neq 0$$
$$0 \text{ for } N = 0$$

- Example:

Find 2's complement representation of 5 (i.e.-5) in 4 –bits

$$5^* = 2^4 - 5$$
$$= 16 - 5 = 11 = 1011_{2's} = \mathbf{1}101 = -5$$

- Two's complement is just a 1 added to 1's complement:

$$2's = 1's + 1$$

- Complement of a complement generates original number



Two's Complement Representation

$$N^* = 2^n - N$$

- Two's complement of +7

2^n	1 0000	
N	0111	(+7)
N^*	1001	(-7)

- Two's complement of -7

2^n	1 0000	
N	1001	(-7)
N^*	0111	(+7)

Shortcut method:

Twos complement = bitwise complement + 1


0111 \rightarrow 1000 + 1 \rightarrow 1001 (representation of -7)

1001 \rightarrow 0110 + 1 \rightarrow 0111 (representation of 7)



Twos Complement Representation

 *like 1's comp
except shifted
one position
clockwise*



$\begin{array}{c} + \\ \swarrow \\ 0\ 100 = +4 \end{array}$
 $\begin{array}{c} - \\ \swarrow \\ 1\ 100 = -4 \end{array}$

- Only one representation for 0
- One more negative number than positive number



Finding 2's Complement

Complement
remaining bits

Copy all bits
to first 1

0	1	0	1	1	0	0	0
1	0	1	0	1	0	0	0

2's complement

Start here

**Table 2-6** Decimal and 4-bit numbers.

<i>Decimal</i>	<i>Two's Complement</i>	<i>Ones' Complement</i>	<i>Signed Magnitude</i>
−8	1000	—	—
−7	1001	1000	1111
−6	1010	1001	1110
−5	1011	1010	1101
−4	1100	1011	1100
−3	1101	1100	1011
−2	1110	1101	1010
−1	1111	1110	1001
0	0000	1111 or 0000	1000 or 0000
1	0001	0001	0001
2	0010	0010	0010
3	0011	0011	0011
4	0100	0100	0100
5	0101	0101	0101
6	0110	0110	0110
7	0111	0111	0111



Range of Numbers

■ 4-bit 2s complement

- $+7 = 0111 = 2^3 - 1$

- $-8 = 1000 = -2^3$

■ 8 bit 2s complement

- $+127 = 01111111 = 2^7 - 1$

- $-128 = 10000000 = -2^7$

■ 16 bit 2s complement

- $+32767 = 01111111 11111111 = 2^{15} - 1$

- $-32768 = 100000000 00000000 = -2^{15}$

■ N bit 2s complement

- $01111111..11111111 = 2^{N-1} - 1$ (largest positive)

- $100000000..00000000 = -2^{N-1}$ (largest negative)



Conversion Between Lengths, e.g. 8 \rightarrow 16

■ Positive number: add leading zeros

□ +18 = 00010010

□ +18 = 00000000 00010010

■ Negative numbers: add leading ones

□ -18 = 11101110

□ -18 = 11111111 11101110

□ i.e. pack with msb (sign bit)

called “sign
extension”



Addition and Subtraction

- $a - b = ?$
- Normal binary addition
- Monitor sign bit of result for overflow

- Take negation of b and add to a
 - i.e. $a - b = a + (-b)$
- So we only need **addition** and **complement** circuits



Addition and Subtraction : Twos Complement

4	0100	-4	1100	
<u>+ 3</u>	<u>0011</u>	<u>+ (-3)</u>	<u>1101</u>	
7	0111	-7	11001	If carry-in to sign = carry-out then ignore carry
4	0100	-4	1100	
<u>- 3</u>	<u>1101</u>	<u>+ 3</u>	<u>0011</u>	
1	10001	-1	1111	
				If carry-in to sign = carry-out then ignore carry

- Simpler addition scheme makes twos complement the most common choice for integer number systems within digital systems





Addition and Subtraction : Twos Complement

- Why can the carry-out be ignored?
- Add 2's complement of N to M
 - This is $M - N = M + N^*$
- If $M \geq N$, will generate carry
 - $M + N^* = M + (2^n - N) = M - N + 2^n$
 - Discard carry: just like subtracting 2^n
 - Result is positive $M - N$
- If $M < N$, no carry



Overflow Conditions

  - Add two positive numbers to get a negative number
- or two negative numbers to get a positive number





Twos Complement Overflow

Expected		0	1	1	1	Actual	
	+5		0	1	0	1	
+	+3		0	0	1	1	
			1	0	0	0	-8

Overflow

Expected		1	0	0	0	Actual	
	-7		1	0	0	1	
+	-2		1	1	1	0	
			0	1	1	1	+7

Overflow

Expected		0	0	0	0	Actual	
	+5		0	1	0	1	
+	+2		0	0	1	0	
			0	1	1	1	+7

No Overflow

Expected		1	1	1	1	Actual	
	-3		1	1	0	1	
+	-5		1	0	1	1	
			1	0	0	0	-8


No Overflow

Overflow when carry in to sign does not equal carry out



Iterative Circuit

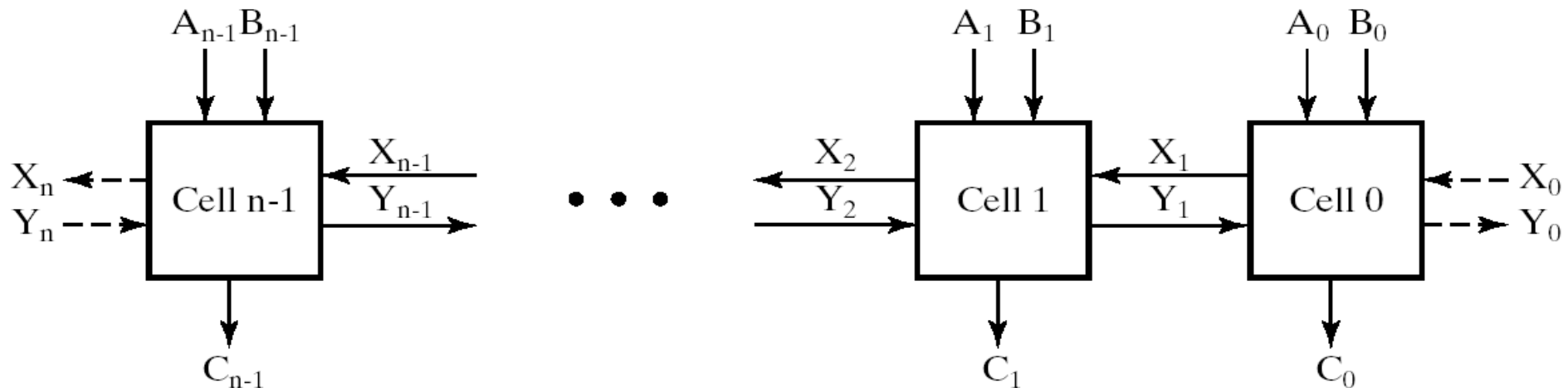- Like a hierarchy, except functional blocks per bit



- Adders are a great example of this type of design
- Design 1-bit circuit, then expand
- Look at
 - Half adder – 2-bit adder, no carry in
 - Inputs are bits to be added
 - Outputs: result and possible carry
 - Full adder – includes carry in, really a 3-bit adder



Half Adder

- Simplest adder block is “half adder”
 - Not very useful by itself


X	Y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

X \ Y	0	1
0	0	0
1	0	1

$$\text{Carry} = XY$$

X \ Y	0	1
0	0	1
1	1	0
 
$$\begin{aligned}\text{Sum} &= X'Y + XY' \\ &= X \oplus Y\end{aligned}$$



Half-adder Schematic



Full Adders

- Basic building block is full adder
- Many full-adders are combined to add more than 1 bits
- Truth table:

X	Y	C _{in}	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



Full Adder

XY		00	01	11	10
C _{in}	0	0	1	0	1
	1	1	0	1	0

$$S = X \oplus Y \oplus C_{in}$$


XY		00	01	11	10
C _{in}	0	0	0	1	0
	1	0	1	1	1

$$\begin{aligned} C_{out} &= XY + XC_{in} + YC_{in} \\ &= XY + (X + Y)C_{in} \end{aligned}$$

- In a multi-stage adder:
 - Variable i indicates stage number.
 - C_{in} is carry to i -th stage, also known as C_i
 - C_{out} is carry to next stage, also known as C_{i+1}



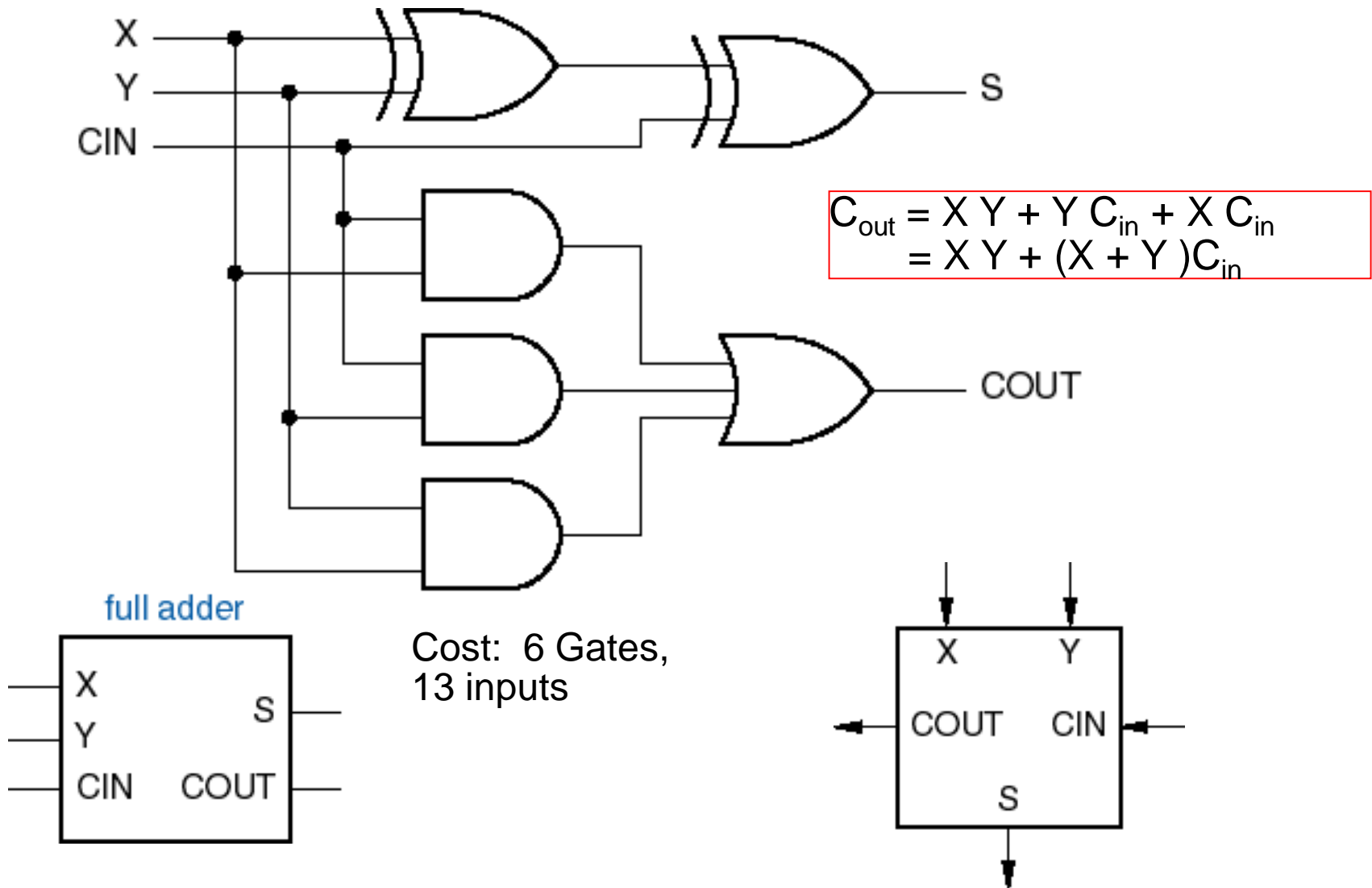
Full-adder circuit: Straightforward Approach





Full Adder: Alternative Implementation

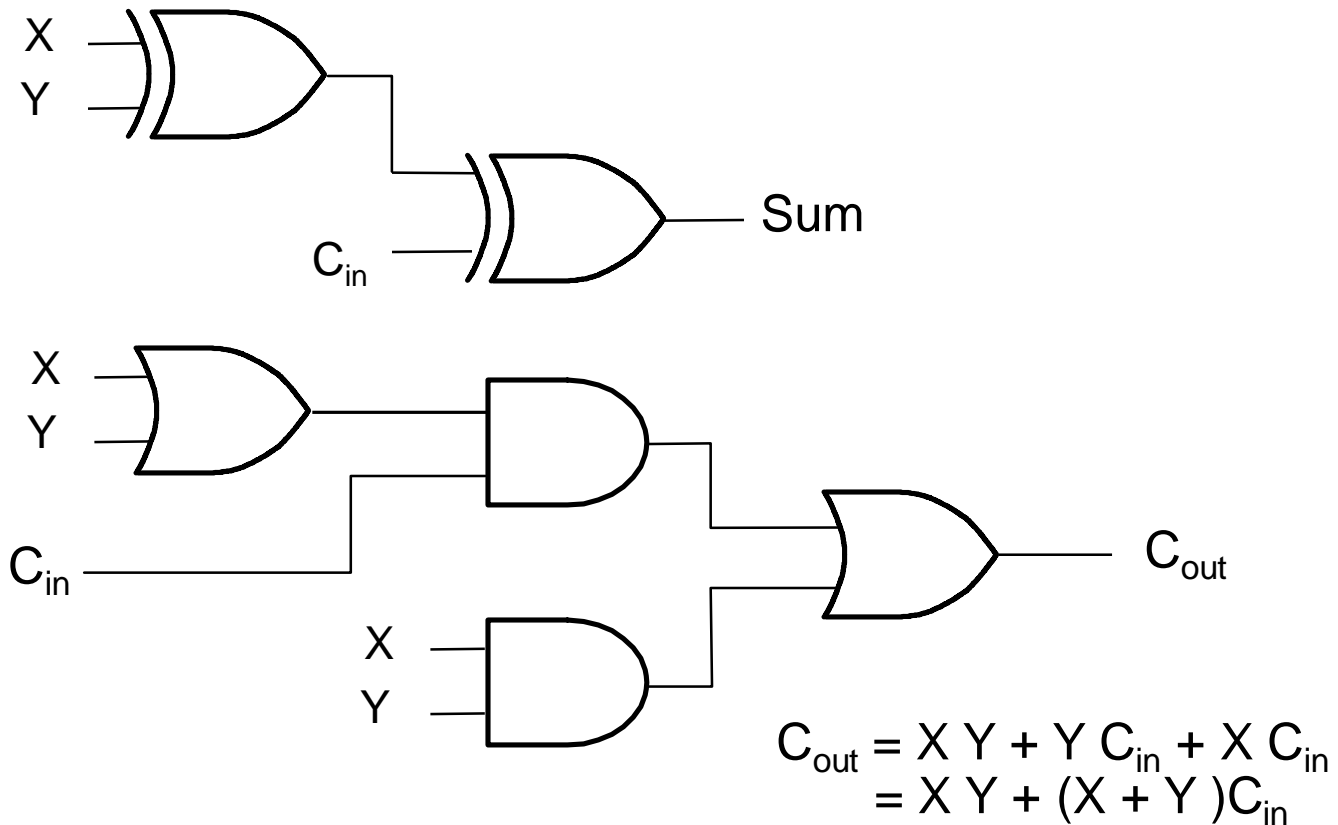- Cost: 6 Gates, max. 2 inputs per gate, 3 levels of logic
- Advantage: All gates of 2-input type, easier to do VLSI layout





Implementation with Two Half Adders (and an OR)

Cost: 5 Gates, 3 levels of logic


 


Fig. 3-27 Logic Diagram of Full Adder

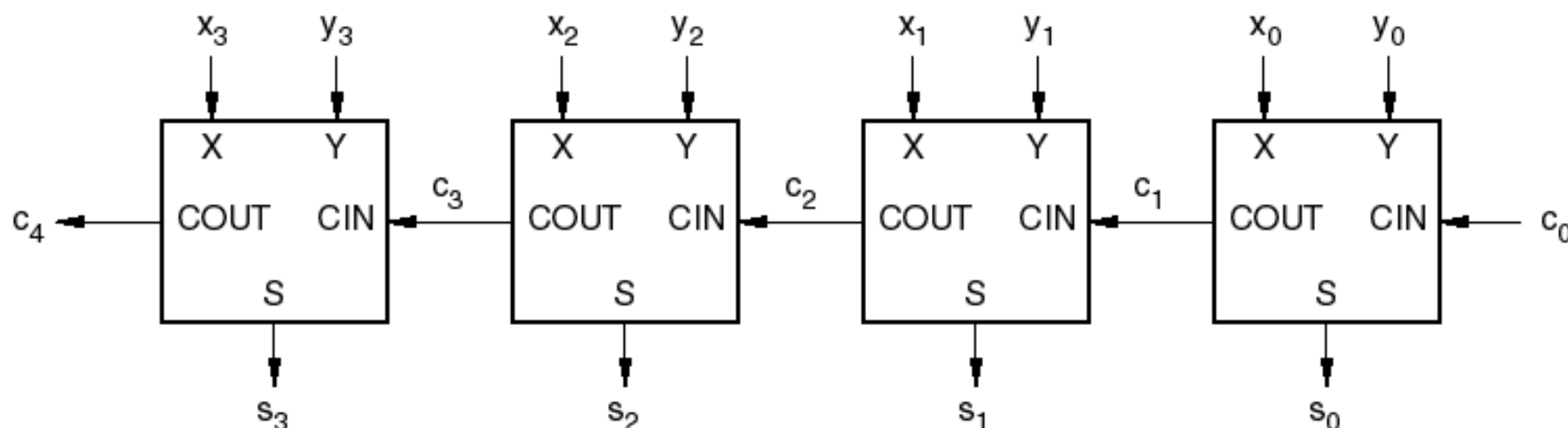


Ripple-Carry Adder




- Straightforward – connect full adders
- Carry-out to carry-in chain
 - C_0 in case this is part of larger chain, maybe just set to zero
- Speed limited by carry chain
- Faster adders eliminate or limit carry chain
 - 2-level AND-OR logic $\implies 2^n$ product terms
 - 3 or 4 levels of logic, carry lookahead



Ripple-Carry Adder

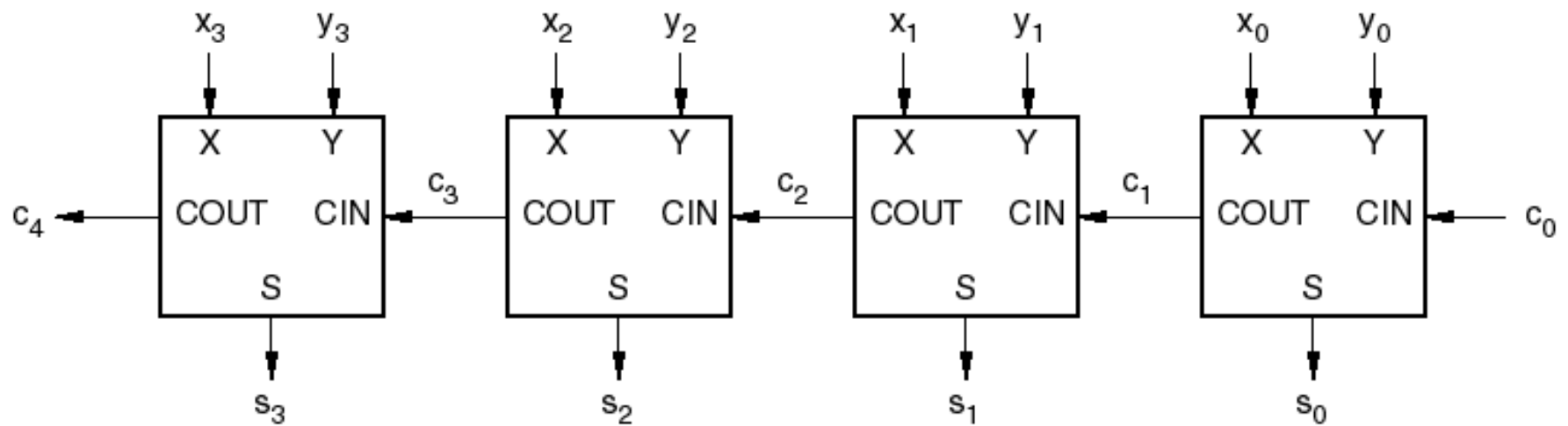


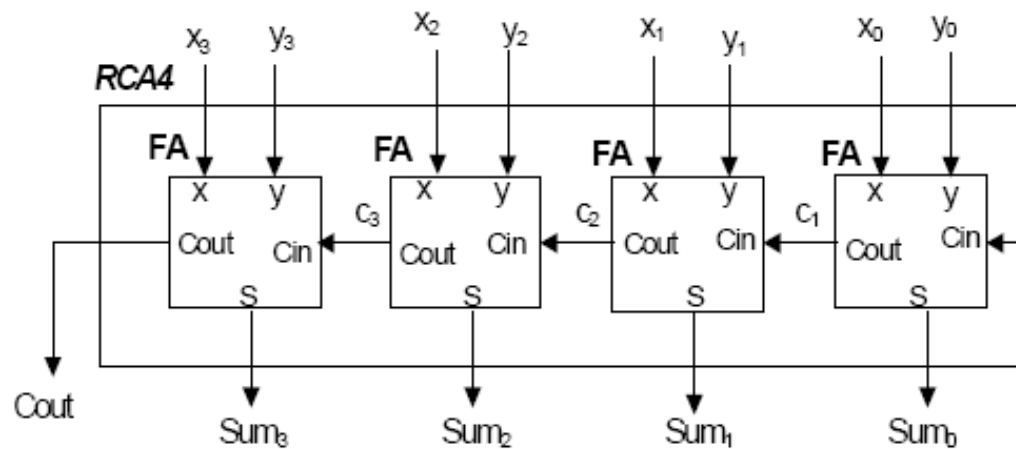

```
module RCA4 (Cin, x, y, Cout, Sum) ;  
    input Cin; input [3:0] x, y; output [3:0] Sum; output Cout;  
    wire c1, c2, c3;  
    FA u0 (.Cin(Cin), .A(x[0]), .B(y[0]), .Sum(Sum[0]), .Cout(c1));  
    FA u1 ( .Cin(c1), .A(x[1]), .B(y[1]), .Sum(Sum[1]), .Cout(c2)) ;  
    FA u2 ( .Cin(c2), .A(x[2]), .B(y[2]), .Sum(Sum[2]), .Cout(c3)) ;  
    FA u3 ( .Cin(c3), .A(x[3]), .B(y[3]), .Sum(Sum[3]), .Cout(Cout)) ;  
endmodule
```



Overflow Detection

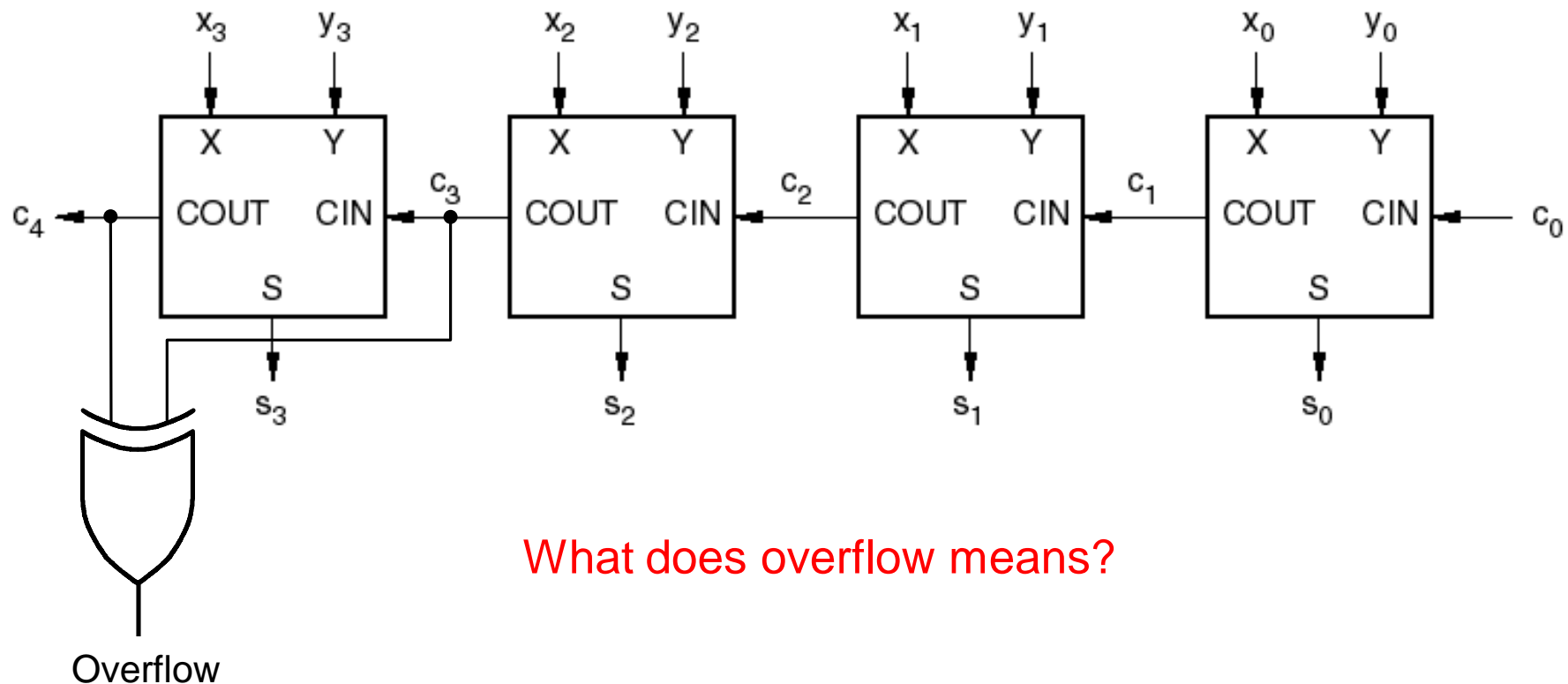

What does overflow means?

- If $\text{Overflow} = 1$, then overflow condition occurs. The output should not be used, i.e. the output is wrong. Condition is that either C_{n-1} or C_n is high, but not both ($n = \text{\#stages}$)



Half Subtractor Circuit


X	Y		B	D
0	0	0 - 0	0	0
0	1	0 - 1	1	1
1	0	1 - 0	0	1
1	1	1 - 1	0	0

D=>Difference

$$D = X'Y + XY' = X \oplus Y$$

B=>Borrow


$$B = X'Y$$

 



Full Subtractor Circuit

X	Y	B _{in}	B _{out}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

 


Difference

$$D = X \oplus Y \oplus B_{in}$$


Borrow out

$$B_{out} = X'Y + X'B_{in} + YB_{in}$$

 




Multi-Stage Full Subtractor

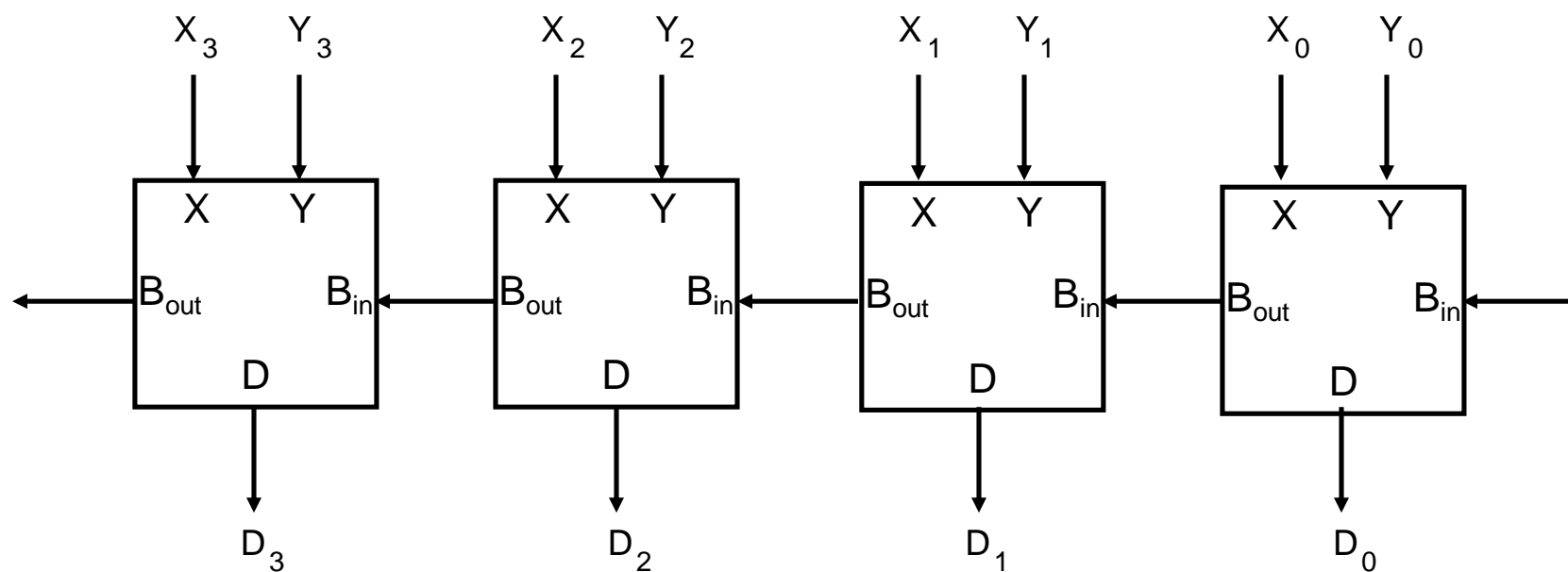



Subtraction Using Adders

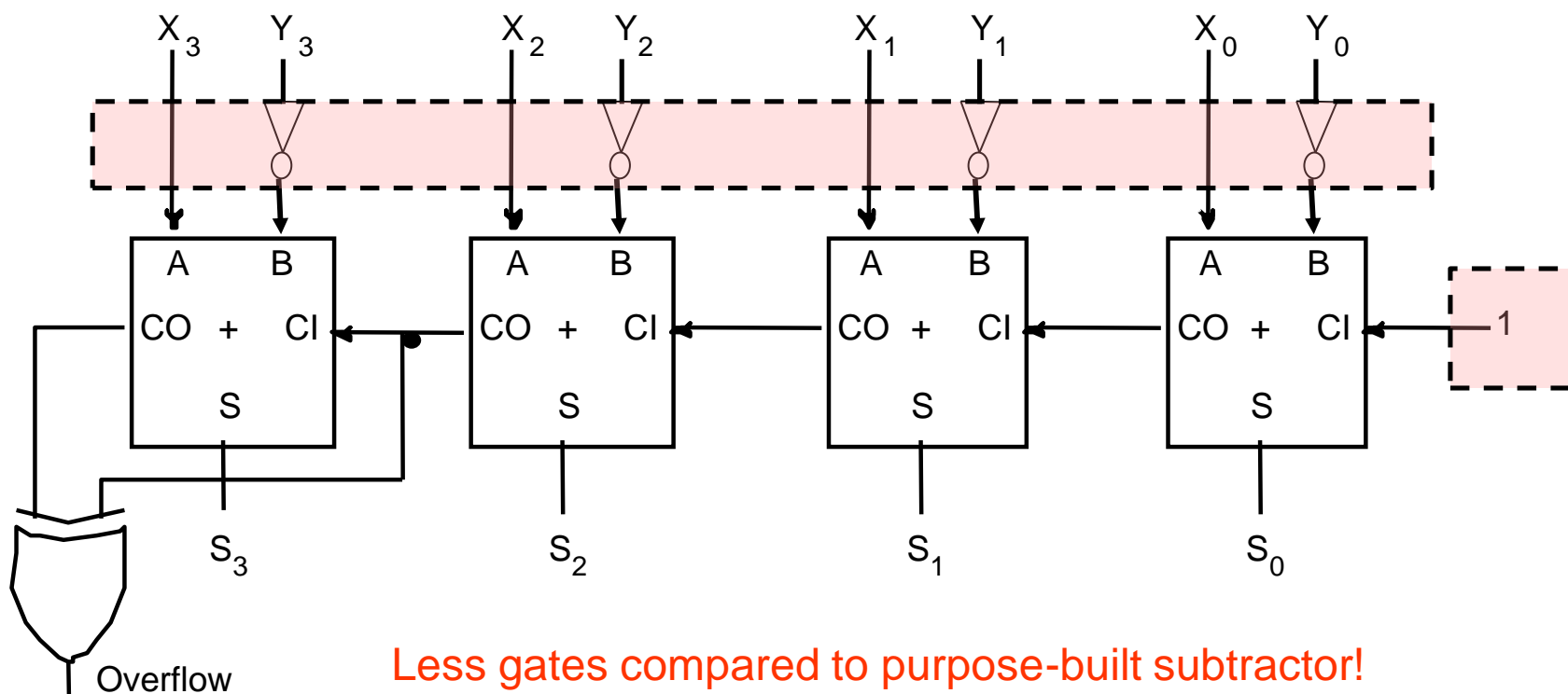
- Subtraction is the same as addition of the two's complement.
- The two's complement is the bit-by-bit complement plus 1.
- Therefore, $X - Y = X + Y' + 1$.
 - Complement Y inputs to adder, set C_1 to 1.



Less gates compared to purpose-built subtractor!



Adder/Subtractor

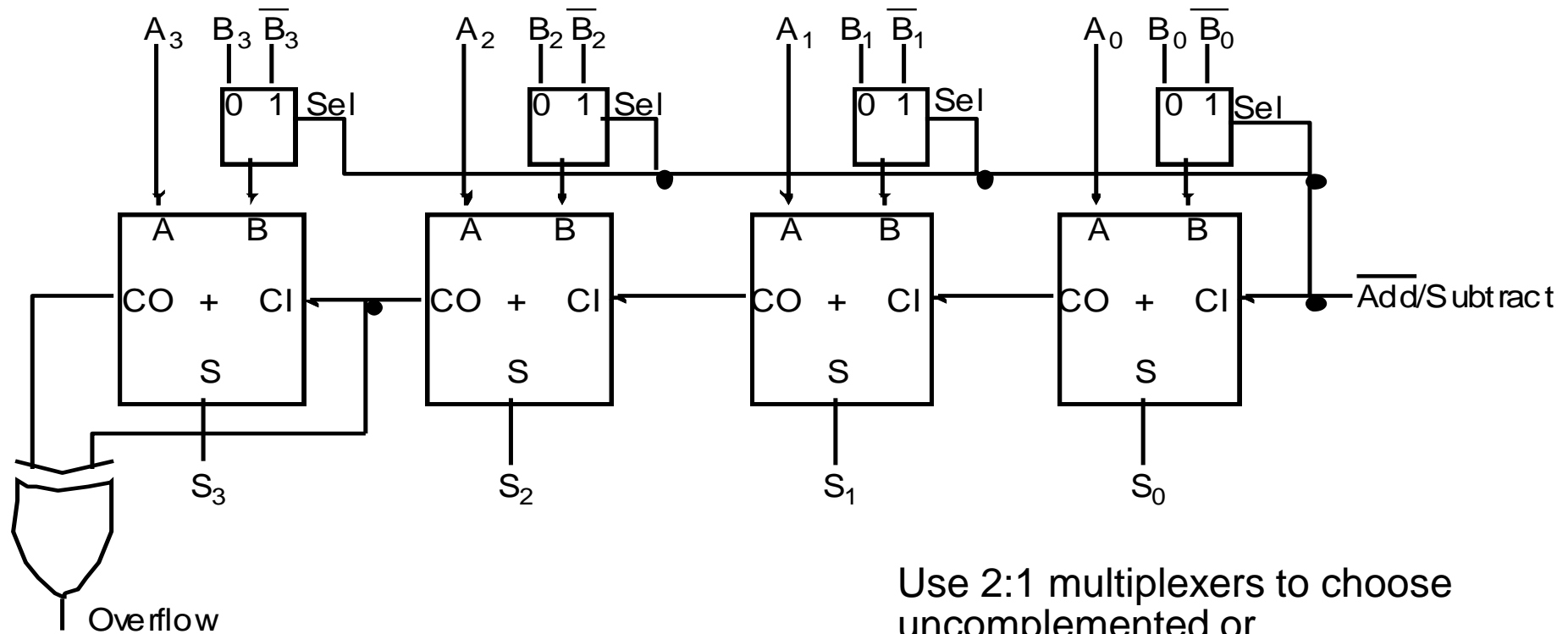

Use 2:1 multiplexers to choose uncomplemented or complemented inputs

Remember, $A - B = A + (-B) = A + \overline{B} + 1$
 So when Add/Sub = 0, $S = A + B$
 When Add/Sub = 1, $S = A + \overline{B} + 1 = A - B$

Why use CO2 xor CO3 as overflow detection?



Alternative Design

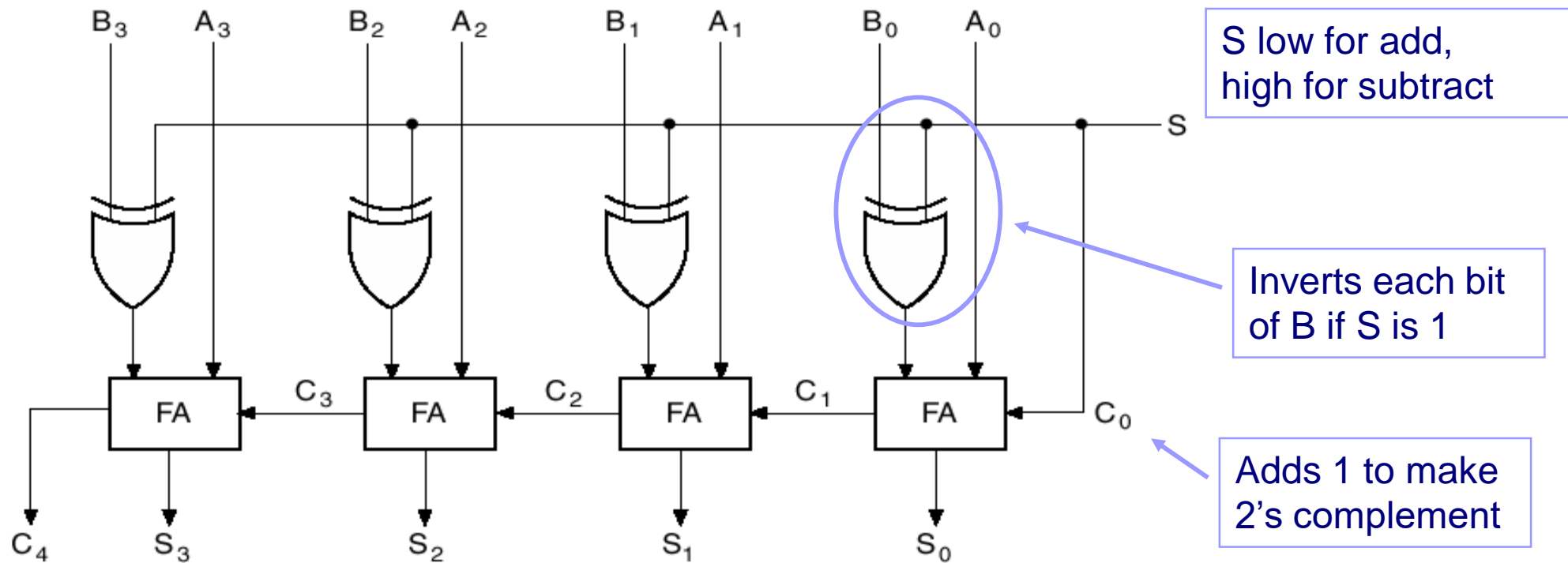


Fig. 3-31 Adder-Subtractor Circuit

- Output is 2's complement if $B > A$