



SMJE 3173

Digital System Design

Introduction to Finite State Machine Design

- Finite State Machine Concept
- Basic Design Procedure
- JASM (Just Another State Machine) Example
- Parity Checker Example
- Counter with Enable Example
- Complex Counter Example



Finite State Machines


- **State**: collection of state variables containing all information from past needed to predict future behavior
- **Finite state machines** (FSMs): circuits that can be in only a fixed number of possible states
- A counter state transition diagram represents simple finite state machines.
 - State = output
 - No choice of sequence
- More generally, in FSM:
 - Next State = function of input and present state
 - Outputs = function of input and present state
 - More complex behavior than counters.
- Finite state machines perform decision-making logic



Concept of the State Machine

Computer Hardware = Datapath + Control

 - FSM generating sequences of control signals
- Instructs datapath what to do next
- Registers
- Combinational Functional Units (e.g., ALU)
- Busses





State Machine Structure

■ State memory:

- n FFs to store current states. All FFs are connected to a common clock signal (i.e. synchronous)

■ Next-state logic:

- determine the next state when state changes occur

■ Output logic:

- determines the output as a function of current state and input


■ There are three models for Finite State Machine (FSM)

- Moore model
- Mealy model
- Synchronous Mealy model

■ What are the differences between all these three models?



Moore Machine

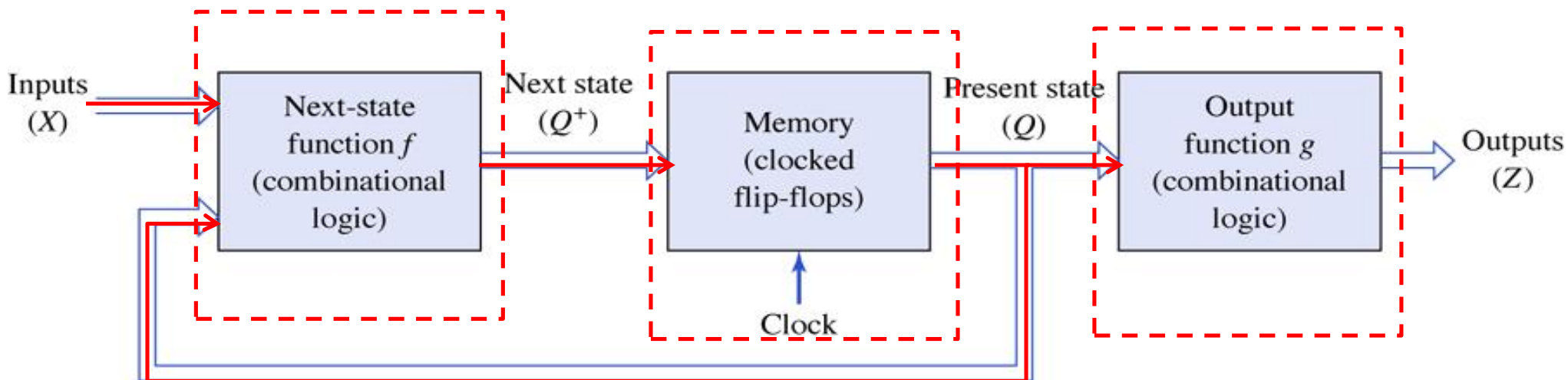

Moore Machine


Outputs are function solely of the current state (present state)

Outputs change synchronously with state changes

Outputs depend on current/present state only



Mealy Machine

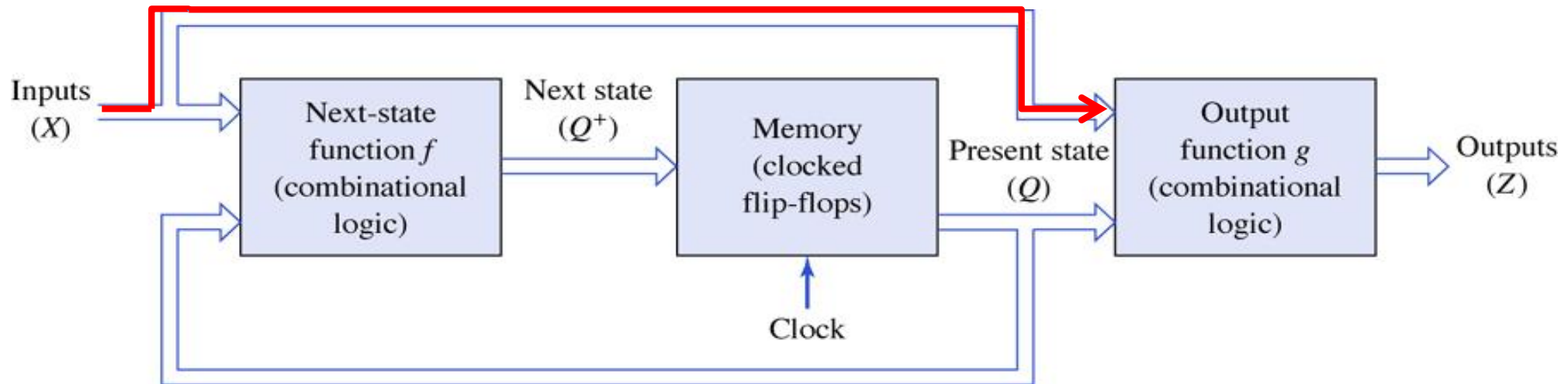

Mealy Machine

Outputs depend on state AND inputs

Asynchronous signals: Input change causes an immediate output change (i.e. output change depends on present state and input to the circuit)



Moore vs Mealy

■ Moore:

- Generally **more** states required to solve a given problem
- **Easier to understand**
- Synchronous output (changes only with a clock pulse) -- The output is delayed in a Moore machine. Output does not occur until the next state change
- Typically take more gates
- Generally easier clocked (generally able to clock faster)
- Easier to simulate using Quartus II

■ Mealy:

- Generally same or less states required
- Slightly more complex to analyze
- Asynchronous output (output can change any time an input changes) may lead to false outputs due to output changing after state changes
- **Generally requires less logic**

Conclusion: Must know both, but learn Moore first




Synchronous Mealy

- Mealy model tend to has glitches in the output.
 - This is due to the asynchronous nature of the Mealy machine.
- Glitches are undesirable in real hardware controllers.
 - But because Mealy machines encode control in fewer states, saving on state register flip-flops, it is still desirable to use them.
- This leads to alternative synchronous design styles for Mealy machines.
- Simply stated, the way to construct a synchronous Mealy machine is to break the direct connection between inputs and outputs by introducing storage elements.



Synchronous Mealy Machine

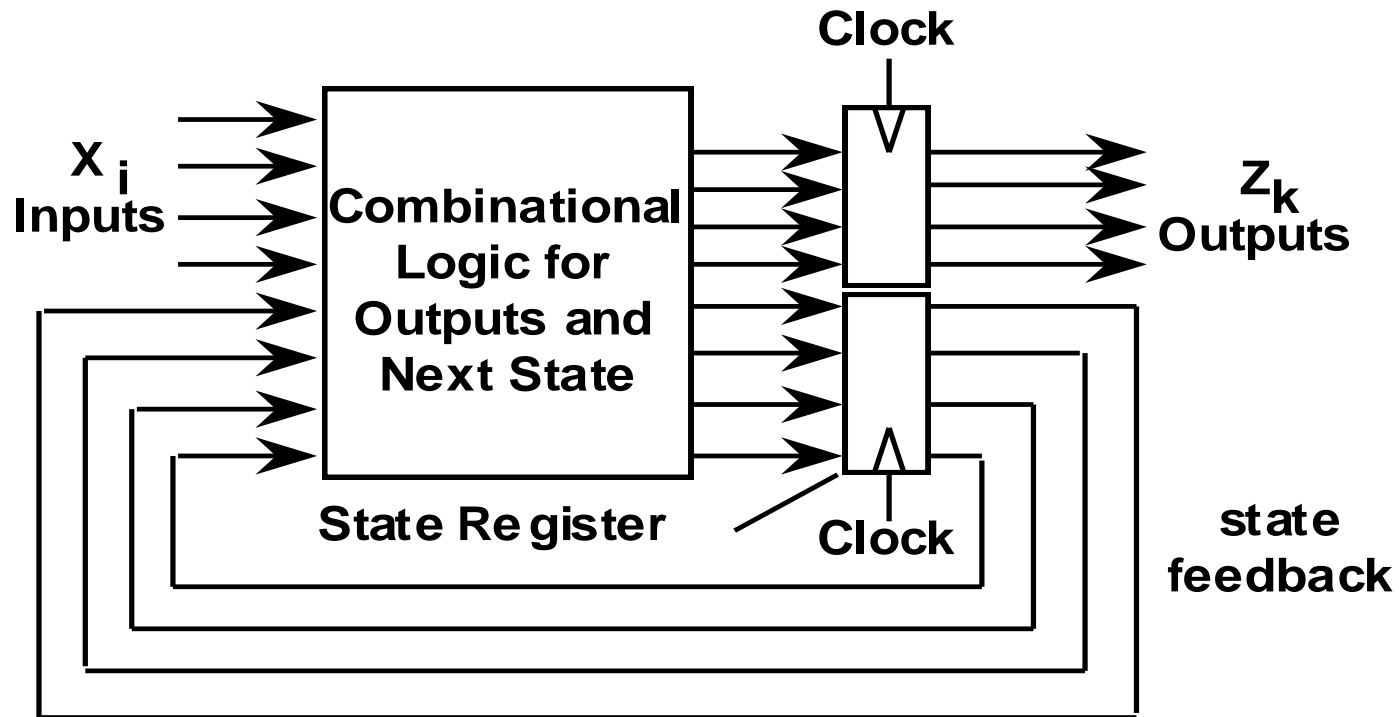

Combination of best ideas of Moore and Mealy:
Less logic + synchronous output


latched state AND outputs

avoids glitchy outputs!



State Machine Timing

- State Time:
 - Time between clocking events.
 - Within the whole clock period
- Clocking event:
 - inputs sampled
 - outputs, next state computed
- After propagation delay
 - outputs stable
 - next state entered
- Moore vs Mealy:
 - Asynchronous signals take effect immediately
 - Synchronous signals take effect at the next clocking event
- Immediate Outputs affect datapath immediately
- Delayed Outputs take effect on next clock edge
 - Important for synchronous Mealy
- For set-up/hold time considerations:
 - Inputs should be stable before clocking event

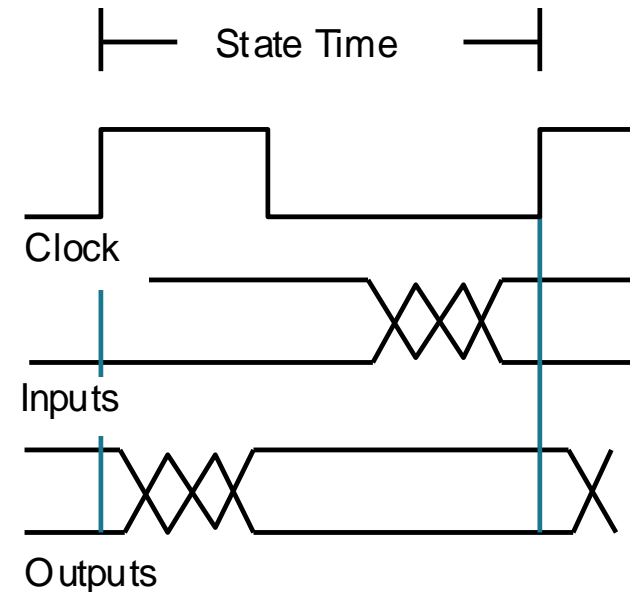



Basic Design Approach

- Eight-step process
 1. Understand the statement of the Specification
 2. Draw a state diagram
 3. Convert state diagram to state table
 4. Optionally, perform state minimization
 5. Perform state assignment
 6. Obtain next state and output equations
 7. Optionally, choose a flip flop type other than DFF and derive the flip flop input maps or tables.
 8. Implement (Draw circuit realization, enter design & verify)



Example 1: Sequence detector for 01 or 10 (Moore Machine)

Mealy and Moore

- **Moore:** outputs depend on current state only (Output does not react immediately to input change)
- **Mealy:** outputs depend on current state and inputs

Mealy and Moore

- Both have:
 - No final state
 - Produce output from an input string
 - No non-determinism
- Mealy machines produce output on transition
- Moore machines produce output on state

Understand the problem specification


| Clock cycle : | t0 | t1 | t2 | t3 | t4 | t5 | t6 | t7 | t8 | t9 | t10 |
|---------------|----|----|----|----|----|----|----|----|----|----|-----|
| input | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| Output: | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |



Example 1: Sequence detector for 01 or 10 (Moore Machine)

1) Draw the complete state diagram:

Start with the expected sequence first

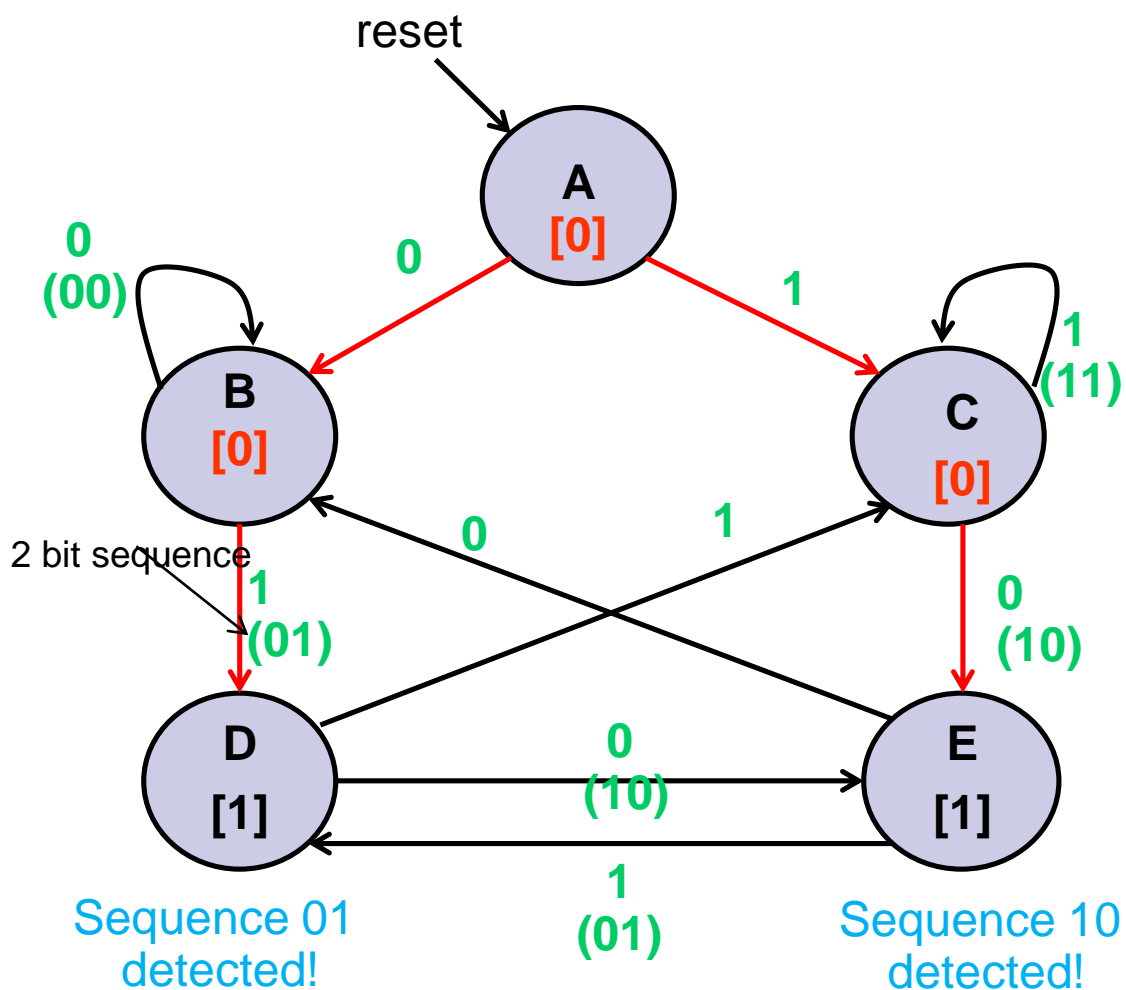

2) Derive state table

| reset | input | current state | next state | output |
|-------|-------|---------------|------------|--------|
| 1 | — | — | A | |
| 0 | 0 | A | B | 0 |
| 0 | 1 | A | C | 0 |
| 0 | 0 | B | B | 0 |
| 0 | 1 | B | D | 0 |
| 0 | 0 | C | E | 0 |
| 0 | 1 | C | C | 0 |
| 0 | 0 | D | E | 1 |
| 0 | 1 | D | C | 1 |
| 0 | 0 | E | B | 1 |
| 0 | 1 | E | D | 1 |

a.k.a. symbolic state table, state name as used in state diagram



■ Step 4: Perform state assignment:

□ Use “simple” binary encoding:

- State ‘A’ >> S0 = 000
- State ‘B’ >> S1 = 001
- State ‘C’ >> S2 = 010
- State ‘D’ >> S3 = 011
- State ‘E’ >> S4 = 100

| Present State | Input | Next State | Output |
|----------------|-------|----------------|--------|
| $PS_2PS_1PS_0$ | IN | $NS_2NS_1NS_0$ | OUT |
| 000 (A) | 0 | 001 (B) | 0 |
| | 1 | 010 (C) | |
| 001 (B) | 0 | 001 (B) | 0 |
| | 1 | 011 (D) | |
| 010 (C) | 0 | 100 (E) | 0 |
| | 1 | 010 (C) | |
| 011 (D) | 0 | 100 (D) | 1 |
| | 1 | 010 (C) | |
| 100 (E) | 0 | 001 (B) | 1 |
| | 1 | 011 (D) | |
| 101 | x | x | x |
| 110 | x | x | x |
| 111 | x | x | x |



Example 1: Sequence detector for 01 or 10 (Mealy Machine)

Mealy and Moore

- **Moore:** outputs depend on current state only (Output does not react immediately to input change)
- **Mealy:** outputs depend on current state and inputs

Mealy and Moore

- Both have:
 - No final state
 - Produce output from an input string
 - No non-determinism
- Mealy machines produce output on transition
- Moore machines produce output on state

Understand the problem specification


| Clock cycle : | t0 | t1 | t2 | t3 | t4 | t5 | t6 | t7 | t8 | t9 | t10 |
|---------------|----|----|----|----|----|----|----|----|----|----|-----|
| input | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| Output: | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |



Example 1: Sequence detector for 01 or 10 (Mealy Machine)

1) Draw the complete state diagram:

Start with the expected sequence first

 

2) Derive state table

| reset | input | current state | next state | output |
|-------|-------|---------------|------------|--------|
| 1 | — | — | A | 0 |
| 0 | 0 | A | B | 0 |
| 0 | 1 | A | C | 0 |
| 0 | 0 | B | B | 0 |
| 0 | 1 | B | C | 1 |
| 0 | 0 | C | B | 1 |
| 0 | 1 | C | C | 0 |

Sequence 10
detected!




■ Step 4: Perform state assignment:

□ Use “simple” binary encoding:

- State ‘A’ >> $S_0 = 00$
- State ‘B’ >> $S_1 = 01$
- State ‘C’ >> $S_2 = 10$

| reset | input | current state | next state | output |
|-------|-------|------------------|---------------|--------|
| 1 | – | – | A | 0 |
| 0 | 0 | A | B | 0 |
| 0 | 1 | A | C | 0 |
| 0 | 0 | B | B | 0 |
| 0 | 1 | B | C | 1 |
| 0 | 0 | C | B | 1 |
| 0 | 1 | C | C | 0 |

 

Encoded State Table

| Present State | Input | Next State | Output |
|------------------|-------|------------|--------|
| PS_1PS_0 | IN | NS_1NS_0 | OUT |
| 00 (A) | 0 | 01 (B) | 0 |
| | 1 | 10 (C) | 0 |
| 01 (B) | 0 | 01 (B) | 0 |
| | 1 | 10 (C) | 1 |
| 10 (C) | 0 | 01 (B) | 1 |
| | 1 | 10 (C) | 0 |



Example 2: JASM (Just Another State Machine)

■ The specification:

- An idle system is activated when an input, **IN** is given. Then, an output, **OUT** is produced after one interval time or cycle later. Next, the system will be back to the idle state, waiting for the next triggering input **IN**.

■ Step 1: Understand the specs.

- Get a sample input/output relationship. More may be needed later.


- Sample input/output relationship:

IN : 001001110

OUT : 000100101

- Draw a simple block diagram and the steps involve.

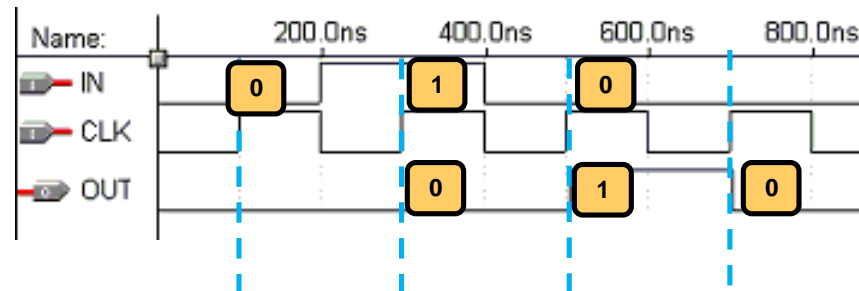
- 1) Activate the system from idle state upon receiving an input; i.e. $IN=1$)
- 2) One cycle later produced an output; i.e. $OUT=1$
- 3) Then return the system to idle state





JASM State Transition Diagram (Moore)

Step 2: Draw state transition diagram

 

Step 3: Derive symbolic state transition table

| Present State | Input | Next State | Output | Comments |
|---------------|-------|------------|--------|---|
| | IN | | OUT | |
| idle | 0 | idle | 0 | Remain in idle state if input does not change |
| | 1 | activate | | Go to next state (activate state) if input is 1 |
| activate | 0 | output | 0 | Go to next state (output state) no matter what the input is. |
| | 1 | output | | |
| output | 0 | idle | 1 | Return to idle state no matter what the input is. Output is high in this state. |
| | 1 | idle | | |



JASM Encoded State Table (Moore)

■ Step 4: Perform state assignment:

- Use of “simple” binary encoding gives us: $S_0 = 00$, $S_1 = 01$ and $S_2 = 10$.
- Must also add in code 11 to take care of don't cares.
- Here, if we somehow get to state 11, next state & output are don't cares.


| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| PS_1PS_0 | IN | NS_1NS_0 | OUT |
| 00 | 0 | 00 | 0 |
| | 1 | 01 | |
| 01 | 0 | 10 | 0 |
| | 1 | 10 | |
| 10 | 0 | 00 | 1 |
| | 1 | 00 | |
| 11 | 0 | 11 | X |
| | 1 | 11 | |



JASM State Transition Diagram (Mealy)

Step 2: Draw state transition diagram

■ Step 3: get symbolic state table.

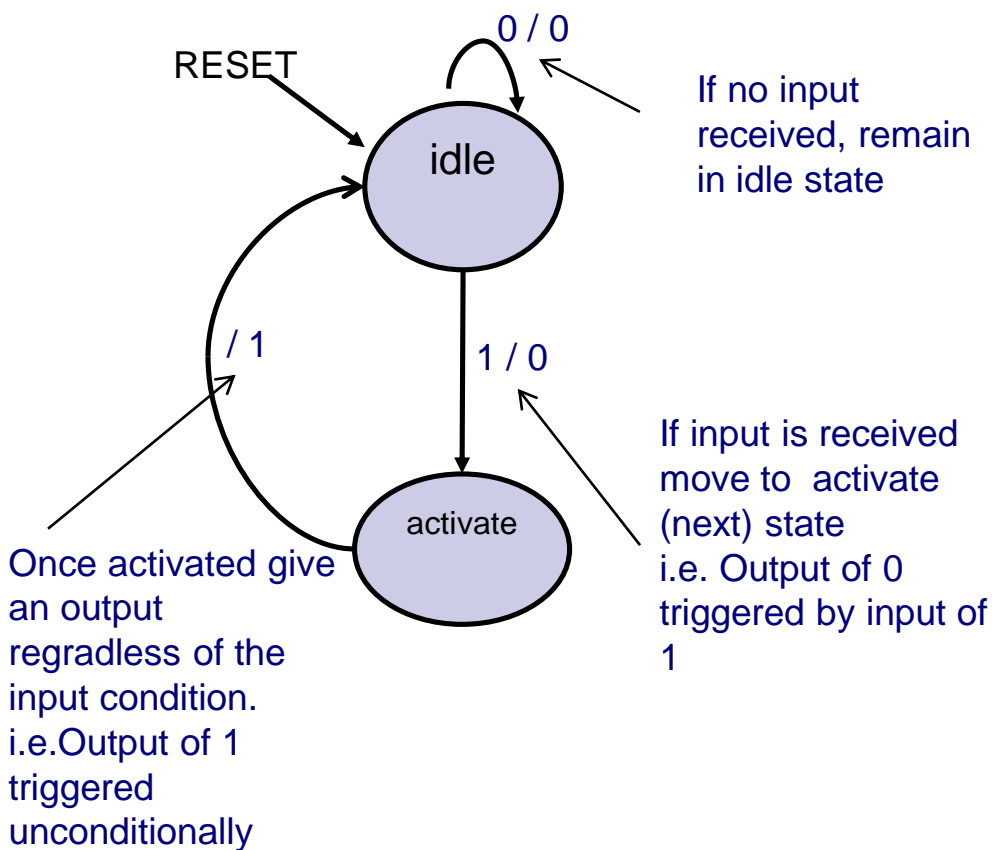

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| | IN | | OUT |
| idle | 0 | idle | 0 |
| | 1 | activate | 0 |
| activate | 0 | idle | 1 |
| | 1 | activate | 1 |

→ idle



JASM Symbolic & Encoded State Table (Mealy)

refer Step 3: symbolic state table.

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| | IN | | OUT |
| idle | 0 | idle | 0 |
| | 1 | activate | 0 |
| activate | 0 | idle | 1 |
| | 1 | idle | 1 |

- Step 4: minimize state transition (SKIP).

Step 5: Perform state assignment

Simple binary encoding of states

Idle : S0 = 00

Activate : S1 = 01

Get encoded state table.

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| PS | IN | NS | OUT |
| 0 | 0 | 0 | 0 |
| | 1 | 1 | |
| 1 | 0 | 0 | 1 |
| | 1 | 0 | |



Example 3: Coin-operated turnstile




From the description, it should be clear that the turnstile is always in exactly 1 of 2 possible states: **Locked** or **Unlocked**.

Problem description

The gate is initially 'locked' and will not rotate to allow a passenger to pass through.

When a coin or token is deposited into the receiver, the gate is "unlocked" but does not turn until the person actually pushes on it and passes through the turnstile, at which time the gate locks until the next coin is deposited.

 The system can be modelled graphically, using rounded rectangles to represent states and arrows to represent transitions between states.



Simple State Machine Model of a Turnstile




Defining Problem Specification

However there are two inputs that affect its transition from one state to the other: putting a coin in the slot (**coin**) and pushing the arm (**push**).

-In the locked state, pushing on the arm has no effect; no matter how many times the input **push** is given, it stays in the locked state.

-Putting a coin in – that is, giving the machine a **coin** input – shifts the state from **Locked** to **Unlocked**. In the unlocked state, putting additional coins in has no effect; that is, giving additional **coin** inputs does not change the state.

 -However, a customer pushing through the arms, giving a **push** input, shifts the state back to **Locked**.





Symbolic state transition table

| Current State | Input | Next State | Output |
|---------------|-------|------------|--|
| Locked | coin | Unlocked | Unlock turnstile so customer can push through |
| | push | Locked | None |
| Unlocked | coin | Unlocked | None |
| | push | Locked | When customer has pushed through, lock turnstile |

Perform state assignment

Simple binary encoding of states

Locked : S0 = 00, Unlocked : S1 = 01

Get encoded state table.

| Present State | Input | Next State | Output |
|------------------|-------|------------------|-----------|
| PS | IN | NS | OUT |
| S0 (Locked) | Coin | S0 (Unlocked) | unlocked |
| | Push | S1 (Locked) | No action |
| S1 (Unlocked) | Coin | S1 (UnLocked) | No action |
| | Push | S1 (Locked) | locked |



Example 2: Bit Sequence Detector (BSD)

■ The specification:

- An input is used to detect a sequence or a series of inputs, 110. When the specific sequence is detected, an output high is produced for a cycle. Then, the system will continue detecting the next sequence.

■ Motivation

- The sequence detector circuit has a practical application in code encoding and decoding such as Huffman codes

■ Step 1: Understand the specs.

- Get a sample input/output relationship.
 - Sample input/output relationship:
IN : 1100011011110...
OUT : 0010000100001...



Example 4: Odd Parity Checker

■ The specification:

- Assert output whenever an input bit stream has odd # of 1's. Output is the same as the state

■ Step 1: Understand the specs.

- Get a sample input/output relationship. (result : 1 = detect || 0= not detected)

- Input bit #1: **0** ←

Output bit #1: 0 >> result = 0 because the number of 1's detected is 0 (even)

- Input bit#2 : 0**1** ←

Output bit #2 : 1 >> result = 1 because the number of 1's detected is 1 (odd)

- Input bit#3: 01**1** ←

Output : 0 >> result = 0 because the number of 1's detected is 2 (even)

- Input bit #4: 011**0** ←

Output : 0 >> result = 0 because the number of 1's detected is 2 (even)

- Input bit#5: 0110**1** ←


Output : 1 >> result = 1 because the number of 1's detected is 3 (odd)

- Input : 01101**0** ←

Output : 1 >> result = 1 because the number of 1's detected is 3 (odd)



Step 2 : Obtain state diagram

 


- circuit is in one of two states.
- transition on each cycle with each new input, over exactly one arc (edge).
- Output depends on which state the circuit is in.

Step 3 : Obtain state table

| Present State | i/p | Next State | o/p |
|---------------|-----|------------|-----|
| Even (S0) | 0 | Even (S0) | 0 |
| Even (S0) | 1 | Odd (S1) | 0 |
| Odd (S1) | 0 | Odd (S1) | 1 |
| Odd (S1) | 1 | Even (S0) | 1 |



Step 4 : Obtain encoded state diagram

 

- Encode : S0 → 0
- Encode : S1 → 1

| Present State | i/p | Next State | o/p |
|---------------|-----|------------|-----|
| 0 (S0) | 0 | 0 (S0) | 0 |
| 0 (S0) | 1 | 1 (S1) | 0 |
| 1 (S1) | 0 | 1 (S1) | 1 |
| 1 (S1) | 1 | 0 (S0) | 1 |


Step 6: Next state & Output Equations

$$NS = PS \oplus INPUT; \quad OUTPUT = PS$$



Odd Parity Checker

 - **Steps 2,3,5:** State Diagram, symbolic state table, & encoded state table



*State
Diagram*

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| Even | 0 | Even | 0 |
| Even | 1 | Odd | 0 |
| Odd | 0 | Odd | 1 |
| Odd | 1 | Even | 1 |

Symbolic State Transition Table

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |

Encoded State Transition Table


Step 6: Next state & Output Equations

$$NS = PS \text{ xor } INPUT; \quad OUTPUT = PS$$




Odd Parity Checker


Steps 7 & 8: Implementation (DFF & TFF)

 

D FF Implementation

 

T FF Implementation

 

Timing Behavior: Input 1 0 0 1 1 0 1 0 1 1 1 0



Example 4: Dual-Mode Counter

Skip !!

- A sync. 3 bit counter has a mode control M. When $M = 0$, the counter counts up in the binary sequence. When $M = 1$, the counter advances through the Gray code sequence.

Step 1 : Understanding the problem specification


- List possible sequences to understand the problem.
 - Binary: 000, 001, 010, 011, 100, 101, 110, 111
 - Gray: 000, 001, 011, 010, 110, 111, 101, 100



Dual-Mode Counter

Step 3,5

Step 2

 

One state for each output combination

Add appropriate arcs for the mode control

State assign:

| | |
|----|-----|
| S0 | 000 |
| S1 | 001 |
| S2 | 010 |
| S3 | 011 |
| S4 | 100 |
| S5 | 101 |
| S6 | 110 |
| S7 | 111 |

Skip !!

| Present State | | | Input | Next State | | |
|---------------|---|---|-------|------------|----|----|
| C | B | A | M | DC | DB | DA |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 |



Dual-Mode Counter

| AM \ CB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | | | |
| 01 | | 1 | | 1 |
| 11 | 1 | 1 | 1 | |
| 10 | 1 | | 1 | 1 |

$$DC = CA'M' + BA'M + CAM + CB'A + C'BAM'$$

| AM \ CB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | | | 1 | 1 |
| 01 | 1 | 1 | 1 | |
| 11 | 1 | 1 | | |
| 10 | | | | 1 |

$$DB = BA' + C'AM + B'AM'$$

Skip !!

| AM \ CB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | 1 | 1 | |
| 01 | 1 | | | |
| 11 | 1 | 1 | 1 | |
| 10 | 1 | | | |

$$DA = A'M' + C'B'M + CBM$$




Dual-mode Counter Circuit

- Exercise:
obtain circuit using state assign
below and TFFs

State assign:

| | |
|----|-----|
| S0 | 000 |
| S1 | 001 |
| S2 | 011 |
| S3 | 010 |
| S4 | 110 |
| S5 | 111 |
| S6 | 101 |
| S7 | 100 |

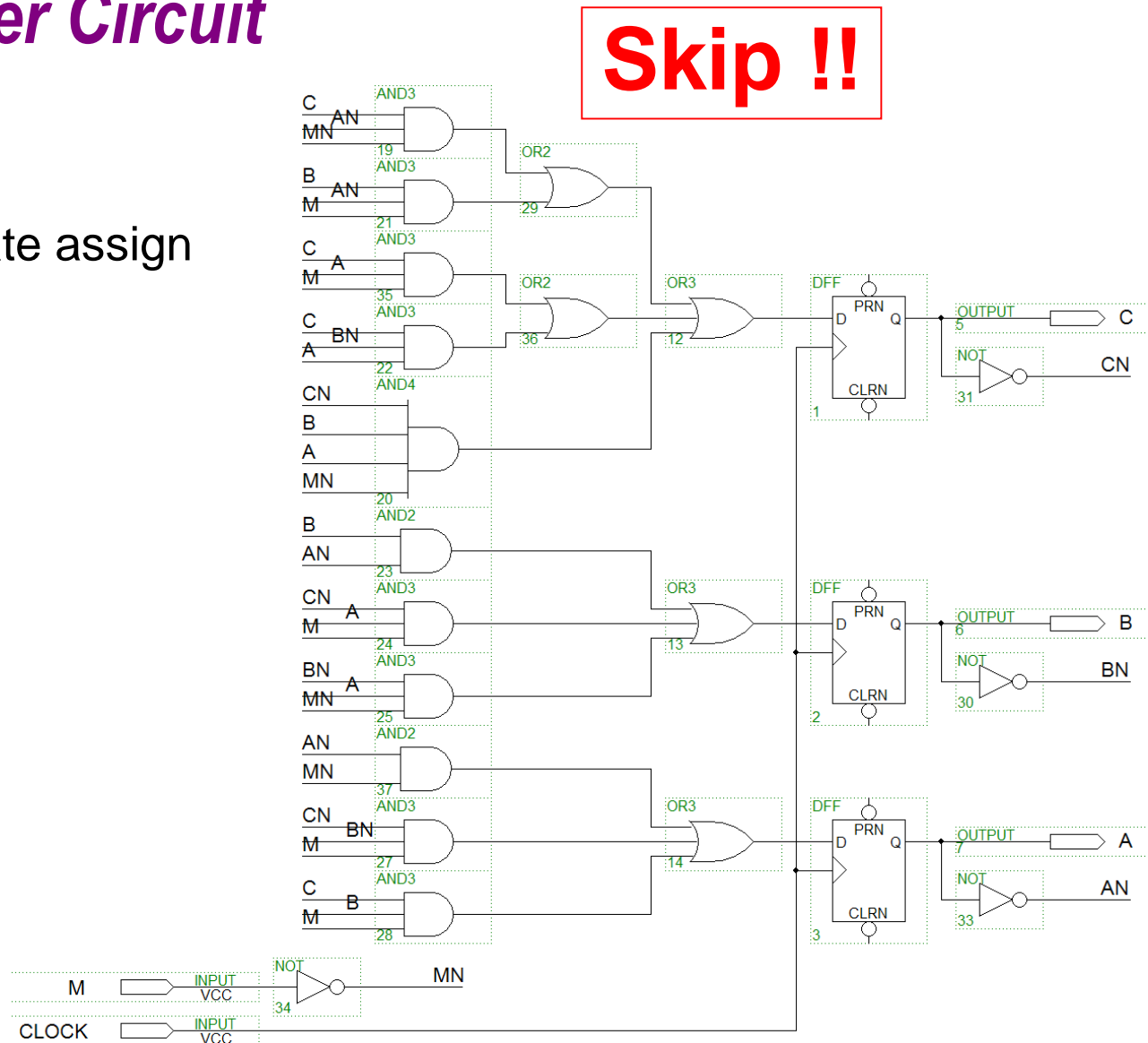



Verilog Construct of FSM-Moore Model

Skip !!


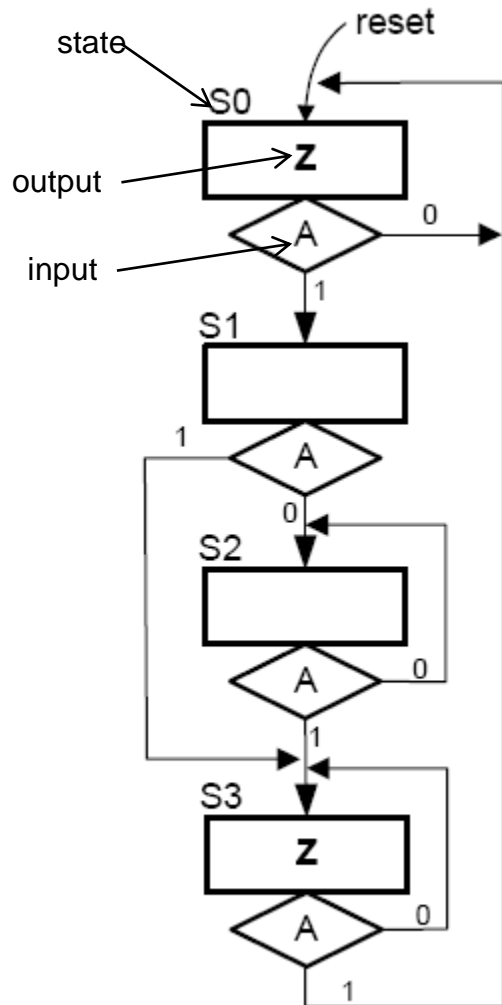


Fig. 5-2a ASM-Chart of FSM1

 


Hardware construct of the FSM

- 1) The FSM has 4 states (S0 – S3) implying that the states variable will be 2 (00 -11).
- 2) Two (2) F/F is required to be form as state register.
- 3) The machine has 1 i/p (A) and 1 o/p (Z)
- 4) The machine is a Moore FSM since output Z only depends on the present state.



Style A: Verilog Construct of FSM -Moore Model

Skip !!

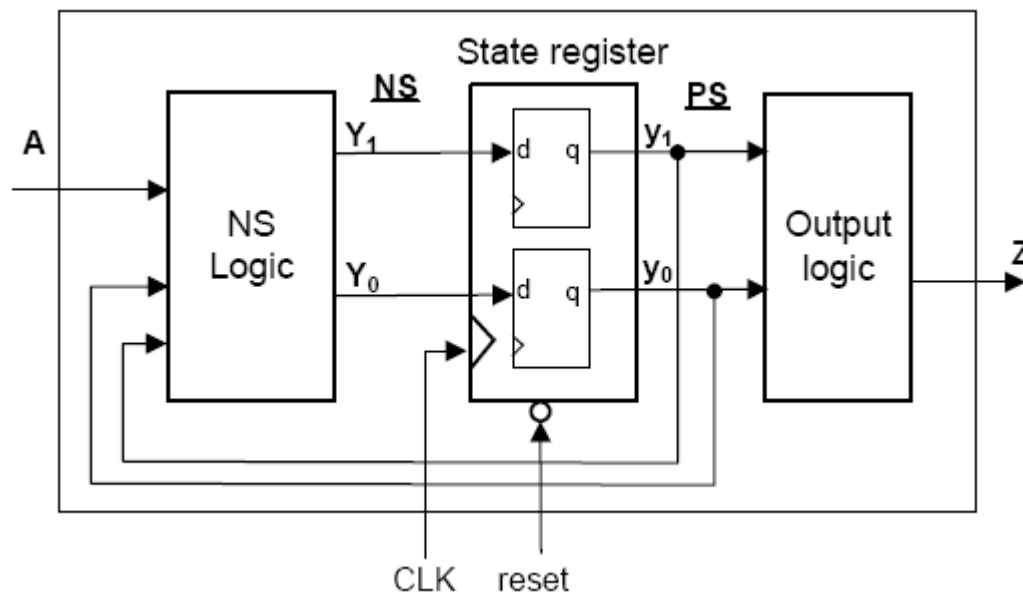

- There are three separate coding segments:
 - one for the *NS logic submodule* (via an **always** block),
 - one for the *state register* (via an **always** block), and
 - one for the *output logic submodule* (via an **assign** statement).



Style A: Verilog Construct of FSM-Moore Model

Skip !!

```
module FSM1 ( A, CLK, reset, y, Z );
    input A, CLK, reset;
    output Z;
    output [1:0] y;
    reg [1:0] y, Y ;

    // state encoding:
    parameter [1:0] S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

    // NS logic submodule:
    always @ (A or y)
        case ( y )
            S0 : if ( A ) Y = S1; else Y = S0;
            S1 : if ( A ) Y = S3;   else Y = S2;
            S2 : if ( A ) Y = S3; else Y = S2;
            S3 : if ( A ) Y = S0; else Y = S3;
        endcase

    // state register submodule:
    always @ ( negedge reset or posedge CLK )
        if (reset == 0) y <= S0 ;
        else y <= Y ;

    // define the Output Logic submodule:
    assign Z = ( y == S0 ) | (y == S3) ;


endmodule
```



JASM Using Mealy Model

Skip !!

- Any system can be defined as Moore machine or Mealy machine but the number of states and the transitions vary.
- The specifications (still remember?):
 - An idle system is activated when an input, **A** is given. Then, an output, **B** is produced after one interval time or cycle later. Next, the system will be back to the idle state, waiting for the next triggering input **A**.
- Step 1: Understand the specs.
 - Been there, done that!
 - Another view of Mealy Model. Notice: $\text{output} = f(\text{input}, \text{present state})$

 




JASM Mealy State Transition Diagram

Skip !!

Step 2: Draw State diagram

 Mealy state diagram is slightly different than Moore's. Next state logic is defined by **Input** ~~outputs~~ too.
i.e. Outputs are associated with state transitions (**arcs**)





JASM Symbolic State Table

- Step 3: get symbolic state table.

Skip !!

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| | IN | | OUT |
| S0 | 0 | S0 | 0 |
| | 1 | S1 | 0 |
| S1 | 0 | S0 | 1 |
| | 1 | S0 | 1 |

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| PS | IN | NS | OUT |
| 0 | 0 | 0 | 0 |
| | 1 | 1 | |
| 1 | 0 | 0 | 1 |
| | 1 | 0 | |

Step 5: Get encoded state table.



Get Logic Equations

- Step 6: Solve the next state & output equations.
- Step 7: Obtain circuit.

| Present State | Input | Next State | Output |
|---------------|-------|------------|--------|
| PS | IN | NS | OUT |
| 0 | 0 | 0 | 0 |
| | 1 | 1 | |
| 1 | 0 | 0 | 1 |
| | 1 | 0 | |

Skip !!

| | | |
|---------|---|---|
| IN \ PS | 0 | 1 |
| 0 | 0 | 0 |
| 1 | 1 | 0 |

$$NS = PS' \bullet IN$$

| | | |
|---------|---|---|
| IN \ PS | 0 | 1 |
| 0 | 0 | 1 |
| 1 | 0 | 1 |

$$OUT = PS$$

- Exercise:
Do step 7 – obtain circuit using TFFs.



Example 2: Bit Sequence Detector (BSD)

■ The specification:

- An input is used to detect a sequence or a series of inputs, 110. When the specific sequence is detected, an output high is produced for a cycle. Then, the system will continue detecting the next sequence inputs.

■ Step 1: Understand the specs.

- Get a sample input/output relationship.

- Sample input/output relationship:

IN : 1100011011110...

OUT : 0010000100001...




110 BSD State Diagram

■ Step 2: Get state diagram

- Start with the expected sequence first
- S0 means 0 bit found, S1 = 1 bit found, S2 = 2 bits found
- If all three bits are detected (110 sequence completed) while in S2, reset (go to S0) while at the same time outputting a 1

IN : 1100011011110...

OUT : 0010000100001...

 



BSD Symbolic State Transition Table

Step 3: Symbolic state table

| Present States | Input | Next States | Output | Comments |
|----------------|-------|-------------|--------|--|
| | IN | | OUT | |
| S0 | 0 | S0 | 0 | Remain in idle state if start sequence is not detected |
| | 1 | S1 | 0 | Go to next state if first bit is detected |
| S1 | 0 | S0 | 0 | Return to starting state if wrong sequence |
| | 1 | S2 | 0 | Go to next state if second bit is detected |
| S2 | 0 | S0 | 1 | Complete sequence is detected, reset & output 1 |
| | 1 | S2 | 0 | Sequence is not completed yet, wait until '0' appears |



BSD Encoded State Table

■ Step 5: Perform state assignment:

□ Use “simple” binary encoding:

- S0 = 00
- S1 = 01
- S2 = 10

| Present State | | Input | Next State | | Output |
|-----------------|-----------------|-------|-----------------|-----------------|--------|
| PS ₁ | PS ₀ | IN | NS ₁ | NS ₀ | OUT |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | X | X | X |
| 1 | 1 | 1 | X | X | X |



BSD Next State & Output Equations

Step 6:

| Present State | | Input | Next State | | Output |
|---------------|--------|-------|------------|--------|--------|
| PS_1 | PS_0 | IN | NS_1 | NS_0 | OUT |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | X | X | X |
| 1 | 1 | 1 | X | X | X |

- Simpler logic compared to Moore version!
- Exercise: Do step 7 – obtain circuit using JKFFs.

| PS_1PS_0 | | | | | |
|------------|--|----|----|----|----|
| IN | | 00 | 01 | 11 | 10 |
| | | 0 | 1 | X | 1 |
| 0 | | 0 | 0 | X | 0 |
| 1 | | 0 | 1 | X | 1 |

$$NS_1 = PS_1 \bullet IN + PS_0 \bullet IN$$

| PS_1PS_0 | | | | | |
|------------|--|----|----|----|----|
| IN | | 00 | 01 | 11 | 10 |
| | | 0 | 1 | X | 0 |
| 0 | | 0 | 0 | X | 0 |
| 1 | | 1 | 0 | X | 0 |

$$NS_0 = PS_1' \bullet PS_0' \bullet IN$$

| PS_1PS_0 | | | | | |
|------------|--|----|----|----|----|
| IN | | 00 | 01 | 11 | 10 |
| | | 0 | 0 | X | 1 |
| 0 | | 0 | 0 | X | 1 |
| 1 | | 0 | 0 | X | 0 |

$$OUT = PS_1 \bullet IN'$$