

Verilog Modeling

1. Modeling Style

2. Verilog Modeling

- Multiplexer
- Decoder
- Encoder

Verilog Modeling Styles

- Dataflow modelling – description of input-output relation of a circuit using continuous assignment statements.
- Behavioural modelling – description of a circuit behaviour using procedural statements.
- Structural modelling – description of a circuit using a set of interconnected components/modules.



Dataflow modeling

- Given a Boolean equation $f = \overline{x1} \cdot \overline{x2} \cdot \overline{x3} + x1 \cdot \overline{x2} \cdot \overline{x3} + x1 \cdot \overline{x2} \cdot x3 + x1 \cdot x2 \cdot x3$

```
module func1 (x1,x2,x3, f);  
    input x1,x2,x3;  
    output f;  
    assign f= (~x1&~x2&~x3) | (x1&~x2&~x3) | (x1&~x2&x3) | (x1&x2&~x3);  
endmodule
```


- how about your 2-bit comparator?

Structural Modeling

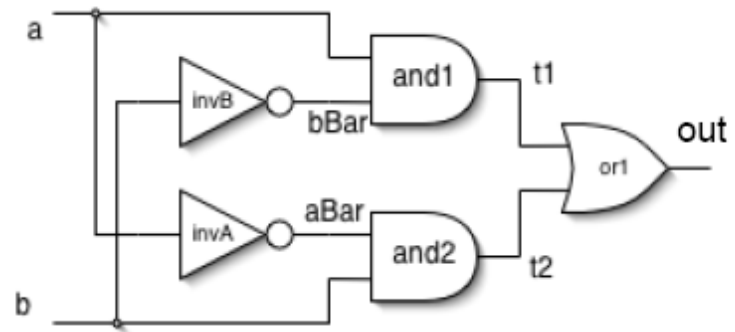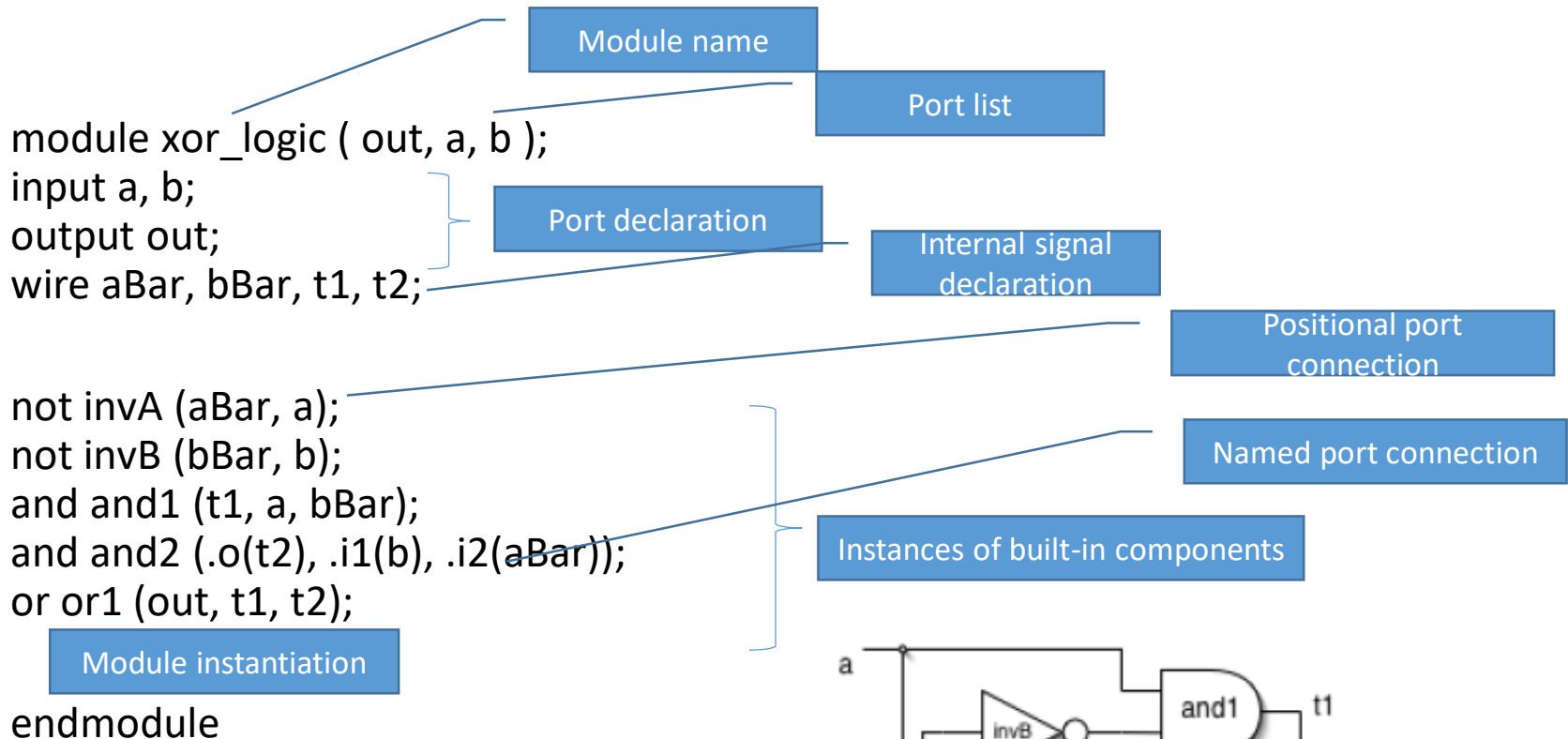

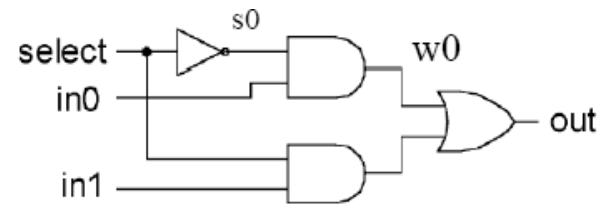Example

```
/* 2-input multiplexor in gates */  
module mux2 (in0, in1, select, out);  
input in0,in1,select;  
output out;  
wire s0,w0,w1;
```



```
not (s0, select);  
and (w0, s0, in0),  
    (w1, select, in1);  
or (out, w0, w1);
```

Multiple instances can share
the same “master” name.

**Better specify
explicitly.**

```
Endmodule          // mux2
```

Behavioural Modeling

```
module OR2(x,y,z);
input x,y;
output z;
reg z;

always@(x or y)
begin
    if((x==0) && (y==0)) z=0;
    else z=1;
end
endmodule
```

```
module mux4 (in0, in1, in2, in3, select,
out);
input in0,in1,in2,in3;
input [1:0] select;
output out;
reg out;

    always @ (in0 in1 in2 in3 select)
        case (select)
            2'b00: out=in0;
            2'b01: out=in1;
            2'b10: out=in2;
            2'b11: out=in3;
        endcase
endmodule // mux4
```

Example

```
module 2mux(in, select, out);  
input [7:0] in;  
input [1:0] select;  
output [1:0] out;  
  
mux4 mux4a( in[0], in[1], in[2], in[3], select, out[0] );  
mux4 mux4b( .select(select), .in0(in[4]), .in1(in[5]),  
in2(in[6]), in3(in[7]),      .out(out[1]) );  
  
endmodule
```


Verilog Modeling

1. Modeling Style

2. Verilog Modeling


- Multiplexer
- Decoder
- Encoder

Multiplexers/Selectors

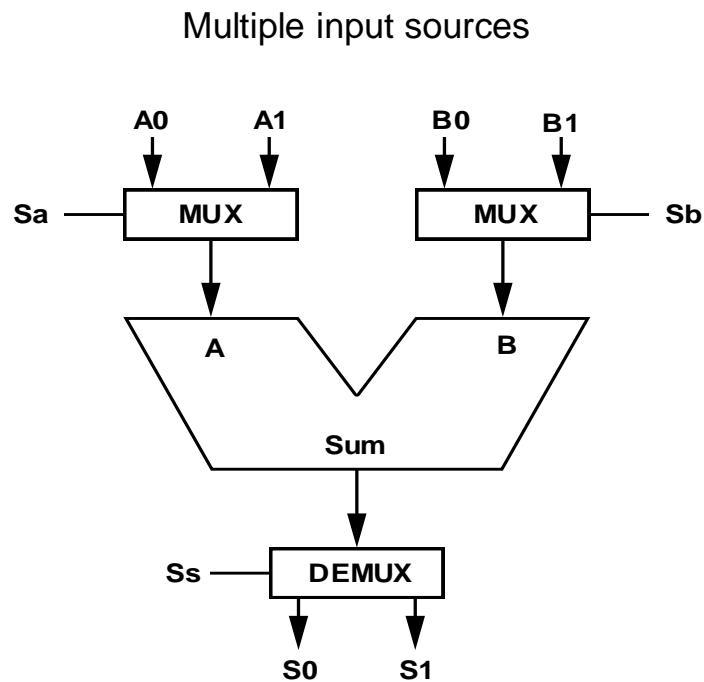

Multiplexers/Selectors: General Concept

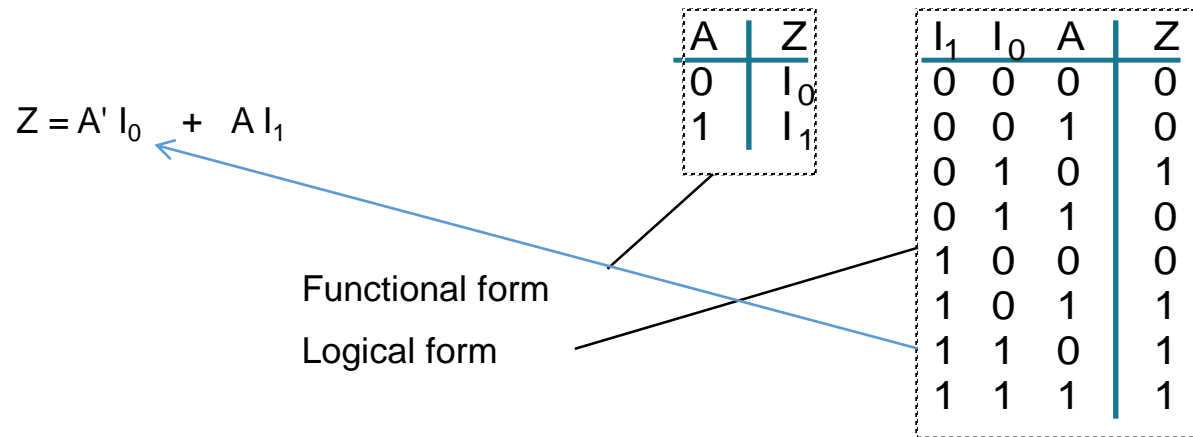- 2^n data inputs, n control inputs, 1 output
- used to connect 2^n points to a single point
- control signal pattern form binary index of input connected to output



*Two alternative forms
for a 2:1 Mux Truth Table*

Mux in verilog

Dataflow Modeling

```
module mux2to1 (i1, i0, a, z);  
input i1, i0, a;  
output z;  
  
    assign z = (~a & i0) | (a & i1);  
  
endmodule
```

Behavioral Modeling


```
module mux2to1 (i1, i0, a, z);  
input i1, i0, a;  
output reg z;  
always @(i1, i0, a) begin  
    if(a) z=i1;  
    else z=i0;  
end  
endmodule
```

if (condition)
 branch1
else branch2

Structural Modeling



```
module mux2to1 (i1, i0, a, z);  
input i1, i0, a;  
output z;  
wire w1,w2, w3;  
    not inv1(w1,a);  
    and and1(w2,w1,i0);  
    and and2(w3,a,i1);  
    or or1(z, w2,w3);  
endmodule
```

Multiplexers/Selectors

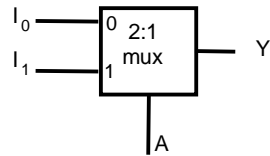


$$Y = A' I_0 + A I_1$$

How about this?

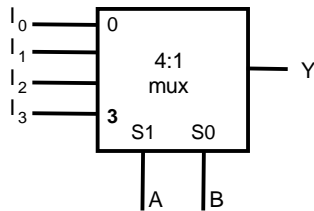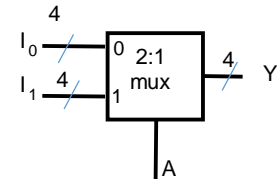
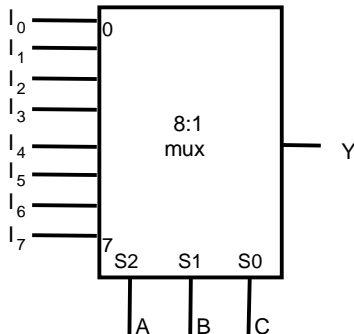
$$Y = A' B' I_0 + A' B I_1 + A B' I_2 + A B I_3$$



$$Y = A' B' C' I_0 + A' B' C I_1 + A' B C' I_2 + A' B C I_3 + A B' C' I_4 + A B' C I_5 + A B C' I_6 + A B C I_7$$


MUX in verilog

```
module mux4to1 (s, in, z);  
  input [1:0] s;  
  input [3:0] in; //e.g. 4-bit bus  
  output reg z;  
  
  always @(s, in)  
  case(s)  
    2'b00: z=in[0];  
    2'b01: z=in[1];  
    2'b10: z=in[2];  
    2'b11: z=in[3];  
  
  endcase  
  
endmodule
```

```
module mux2to1 (i1, i0, a, z);  
input i1, i0, a;  
output z;  
wire w1,w2, w3;
```

```
module mux4to1 (s, in, z);  
  input [1:0] s;  
  input [3:0] in;  
  output reg z;  
  wire w1, w2;  
  mux2to1 mux1(i[3], i[2], s[0], w1 );  
  mux2to1 mux2(i[1], i[0], s[0], w2 );  
  mux2to1 mux3(w1, w2, s[1], z);  
endmodule
```


Multiplexer/Selector: Expansion

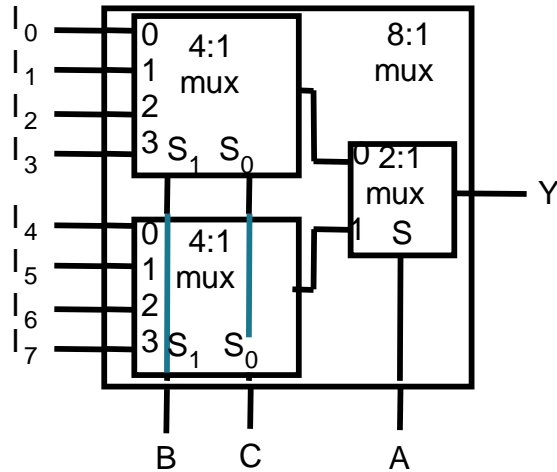

Alternative 8:1 Mux Implementation

Control signals B and C simultaneously choose one of I_0 - I_3 and I_4 - I_7

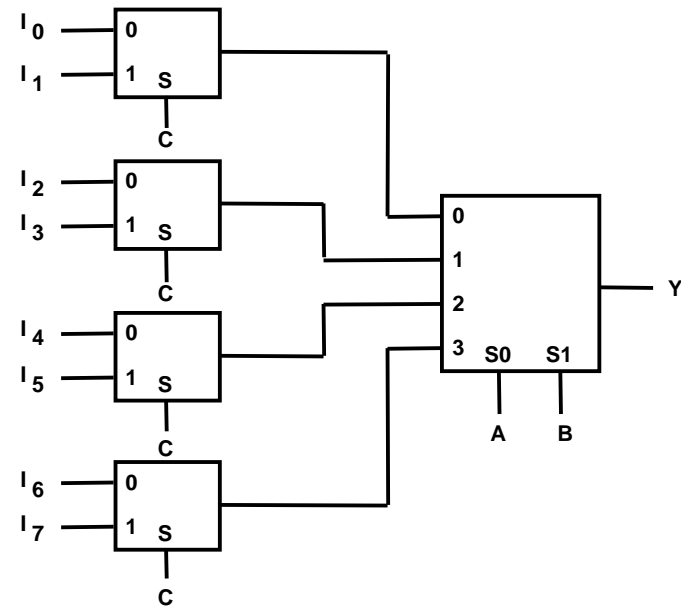Control signal A chooses which of the upper or lower MUX's output to gate to Y



Issue : implied memory

□ **reg :**

variable retains old value when the variable is not assigned a new value under some condition.

□ **Example:**

```
module mux4to1(en,x,z);  
input en,x;  
output reg z;  
always @(en or x)  
if(en)  
    z=x;  
endmodule
```


Multiplexer/Selector: Implementing logic functions

$2^{n-1} : 1$ multiplexer can implement any function of n variables


$n-1$ control variables; remaining variable is a data input to the mux

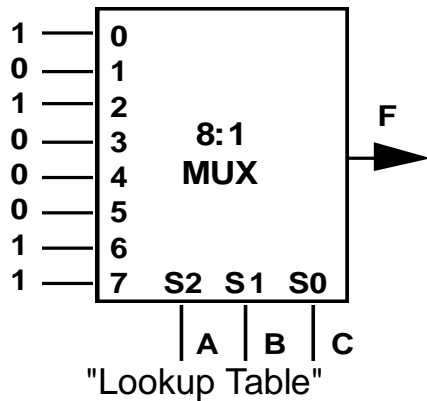Example:

$$\begin{aligned} F(A,B,C) &= m_0 + m_2 + m_6 + m_7 \\ &= A' B' C' + A' B C' + A B C' + A B C \\ &= A' B' (C') + A' B (C') + A B' (0) + A B (1) \end{aligned}$$




A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

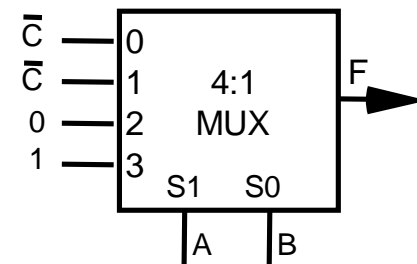



Decoders

- General decoder structure

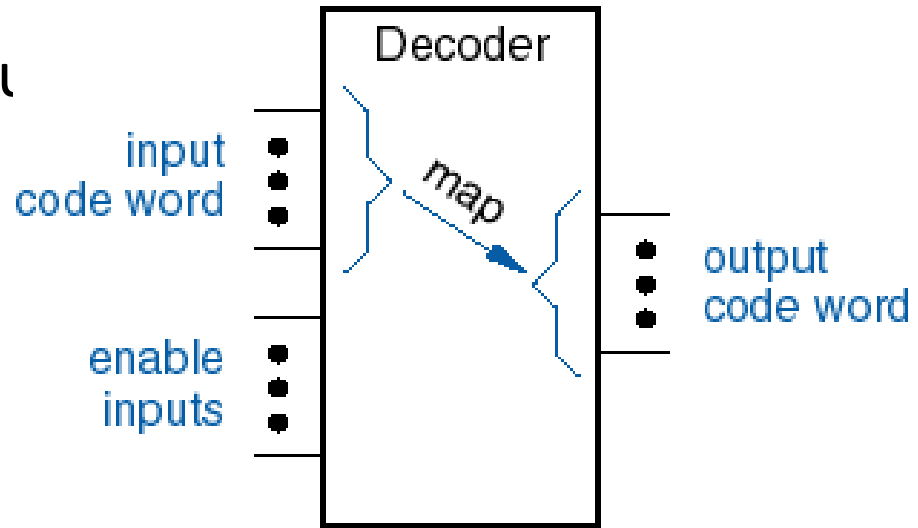

- Typically n inputs, 2^n outputs
 - 2-to-4, 3-to-8, 4-to-16, etc
- Control inputs (called select S) represent Binary index of output to which the input is connected
- Data input usually called "enable" (G).

Binary 2-to-4 decoder

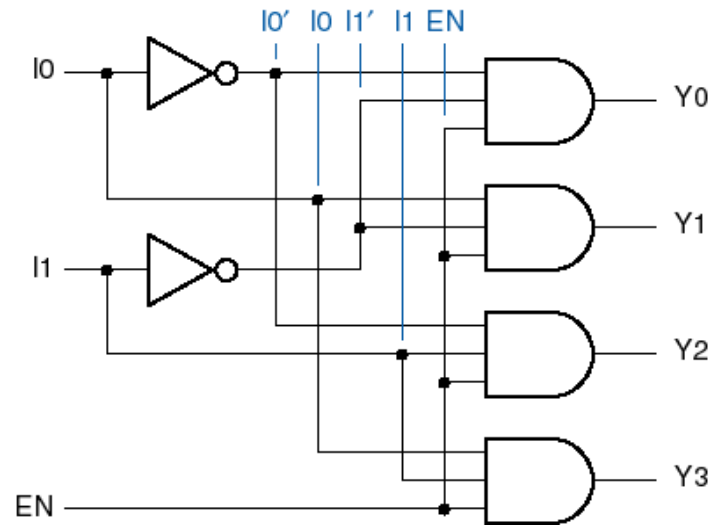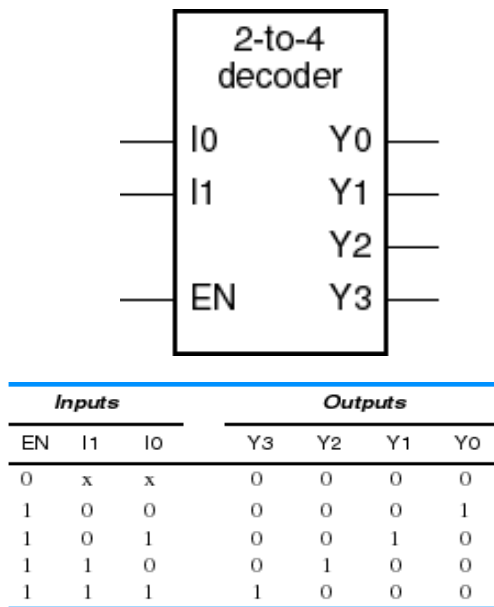

Note "x" (don't care) notation.

Decoder in Verilog #1

```
module decoder2by4_using_case (i, y, en);  
input [1:0] i ;  
input en ;  
output reg [3:0] y ;
```

```
always @ (en or i)
```

```
begin
```

```
  y = 0;
```

```
  if (en) begin
```

```
    case (i)
```

```
      2'h0 : y = 4'h1;
```

```
      2'h1 : y = 4'h2;
```

```
      2'h2 : y = 4'h4;
```

```
      2'h3 : y = 4'h8;
```

```
    endcase
```

```
  end
```

```
end
```

```
endmodule
```

Watch out the pairs !

begin - end

case – endcase

module – endmodule ,,,

```
// or [y3 y2 y1 y0] = 0001
```

```
// or [y3 y2 y1 y0] = 0010
```

```
// or [y3 y2 y1 y0] = 0100
```

```
// or [y3 y2 y1 y0] = 1000
```

Decoder in Verilog #2

```

22 wire [2:0] C;
23
24 assign LEDR = SW;
25 assign C[2:0] = SW[2:0];
26
27 /*
28  *      0
29  *      ---
30  *      |   |
31  *      5|   |1
32  *      | 6 |
33  *      ---
34  *      |   |
35  *      4|   |2
36  *      |   |
37  *      ---
38  *      3
39  */
40 // the following equations describe HEX0[0-6] in canonical SOP form
41 assign HEX0[0] = ~( (~C[2] & ~C[1] & C[0]) | (~C[2] & C[1] & C[0]));
42 assign HEX0[1] = ~( (~C[2] & ~C[1] & ~C[0]) | (~C[2] & C[1] & C[0]));
43 assign HEX0[2] = ~( (~C[2] & ~C[1] & ~C[0]) | (~C[2] & C[1] & C[0]));
44 assign HEX0[3] = ~( (~C[2] & ~C[1] & C[0]) | (~C[2] & C[1] & ~C[0]) |
45   (~C[2] & C[1] & C[0]));
46 assign HEX0[4] = ~( (~C[2] & ~C[1] & ~C[0]) | (~C[2] & ~C[1] & C[0]) |
47   (~C[2] & C[1] & ~C[0]) | (~C[2] & C[1] & C[0]));
48 assign HEX0[5] = ~( (~C[2] & ~C[1] & ~C[0]) | (~C[2] & ~C[1] & C[0]) |
49   (~C[2] & C[1] & ~C[0]) | (~C[2] & C[1] & C[0]));
50 assign HEX0[6] = ~( (~C[2] & ~C[1] & ~C[0]) | (~C[2] & ~C[1] & C[0]));
51 endmodule


```

```

1 // Implements a circuit that can display five characters on a 7-segment
2 // display.
3 // inputs: SW2-0 selects the letter to display. The characters are:
4 //      SW 2 1 0      Char
5 //      -----
6 //      0 0 0      'H'
7 //      0 0 1      'E'
8 //      0 1 0      'L'
9 //      0 1 1      'O'
10 //      1 0 0      ' ' Blank
11 //      1 0 1      ' ' Blank
12 //      1 1 0      ' ' Blank
13 //      1 1 1      ' ' Blank
14 //
15 // outputs: LEDR2-0 show the states of the switches
16 //      HEX0 displays the selected character
17 module pro3 (SW, LEDR, HEX0);
18     input [2:0] SW;           // toggle switches
19     output [2:0] LEDR;        // red LEDs
20     output [0:6] HEX0;        // 7-seg display
21
22     wire [2:0] C;
23
24     assign LEDR = SW;
25     assign C[2:0] = SW[2:0];

```

8-to-3 Bit Priority Encoder

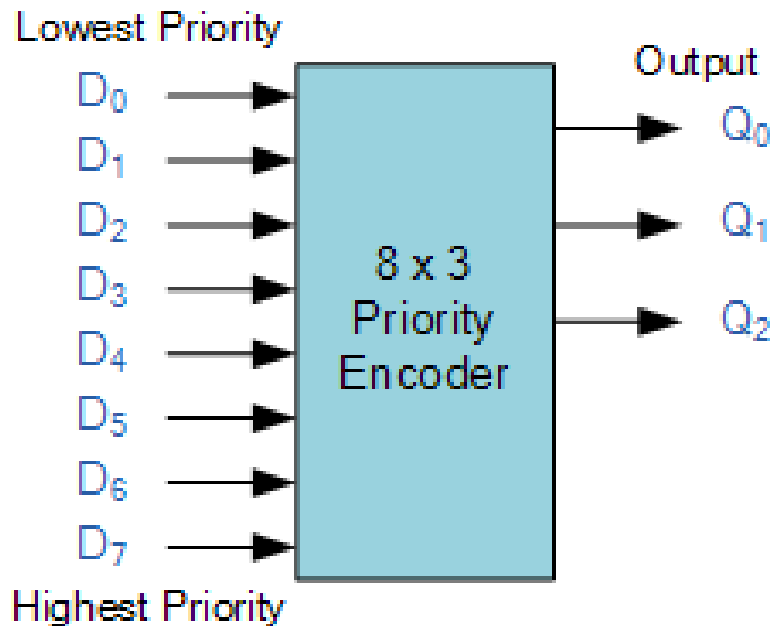

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1

X = don't care


The priority encoders output corresponds to the currently active input which has the highest priority.

If input lines “D2“, “D3” and “D5” are applied simultaneously the output code would be for input “D5” (“101”) as this has the highest order out of the 3 inputs.

Outputs are calculated as:

Inputs									Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀		Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1		0	0	0
0	0	0	0	0	0	1	x		0	0	1
0	0	0	0	0	1	x	x		0	1	0
0	0	0	0	1	x	x	x		0	1	1
0	0	0	1	x	x	x	x		1	0	0
0	0	1	x	x	x	x	x		1	0	1
0	1	x	x	x	x	x	x		1	1	0
1	x	x	x	x	x	x	x		1	1	1

X = dont care

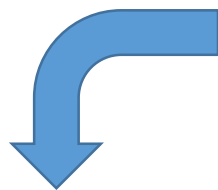

Output Q₀

$$\begin{aligned}
 Q_0 &= \Sigma(1, 3, 5, 7) \\
 &= \Sigma(\bar{D}_7\bar{D}_6\bar{D}_5\bar{D}_4\bar{D}_3\bar{D}_2D_1 + \bar{D}_7\bar{D}_6\bar{D}_5\bar{D}_4D_3 + \bar{D}_7\bar{D}_6D_5 + D_7) \\
 &= \Sigma(\bar{D}_6\bar{D}_4\bar{D}_2D_1 + \bar{D}_6\bar{D}_4D_3 + \bar{D}_6D_5 + D_7) \\
 &= \Sigma(\bar{D}_6(\bar{D}_4\bar{D}_2D_1 + \bar{D}_4D_3 + D_5) + D_7)
 \end{aligned}$$

Output Q₁

$$\begin{aligned}
 Q_1 &= \Sigma(2, 3, 6, 7) \\
 &= \Sigma(\bar{D}_7\bar{D}_6\bar{D}_5\bar{D}_4\bar{D}_3D_2 + \bar{D}_7\bar{D}_6\bar{D}_5\bar{D}_4D_3 + \bar{D}_7D_6 + D_7) \\
 &= \Sigma(\bar{D}_5\bar{D}_4D_2 + \bar{D}_5\bar{D}_4D_3 + D_6 + D_7) \\
 &= \Sigma(\bar{D}_5\bar{D}_4(D_2 + D_3) + D_6 + D_7)
 \end{aligned}$$

Output Q₂

$$\begin{aligned}
 Q_2 &= \Sigma(4, 5, 6, 7) \\
 &= \Sigma(\bar{D}_7\bar{D}_6\bar{D}_5D_4 + \bar{D}_7\bar{D}_6D_5 + \bar{D}_7D_6 + D_7) \\
 &= \Sigma(D_4 + D_5 + D_6 + D_7)
 \end{aligned}$$

$$\begin{aligned}
 Q_0 &= \Sigma(\bar{D}_6(\bar{D}_4\bar{D}_2D_1 + \bar{D}_4D_3 + D_5) + D_7) \\
 Q_1 &= \Sigma(\bar{D}_5\bar{D}_4(D_2 + D_3) + D_6 + D_7) \\
 Q_2 &= \Sigma(D_4 + D_5 + D_6 + D_7)
 \end{aligned}$$


8-to-3 Bit Priority Encoder

$$Q_0 = \sum \left(\bar{D}_6 \left(\bar{D}_4 \bar{D}_2 D_1 + \bar{D}_4 D_3 + D_5 \right) + D_7 \right)$$

$$Q_1 = \sum \left(\bar{D}_5 \bar{D}_4 (D_2 + D_3) + D_6 + D_7 \right)$$

$$Q_2 = \sum (D_4 + D_5 + D_6 + D_7)$$

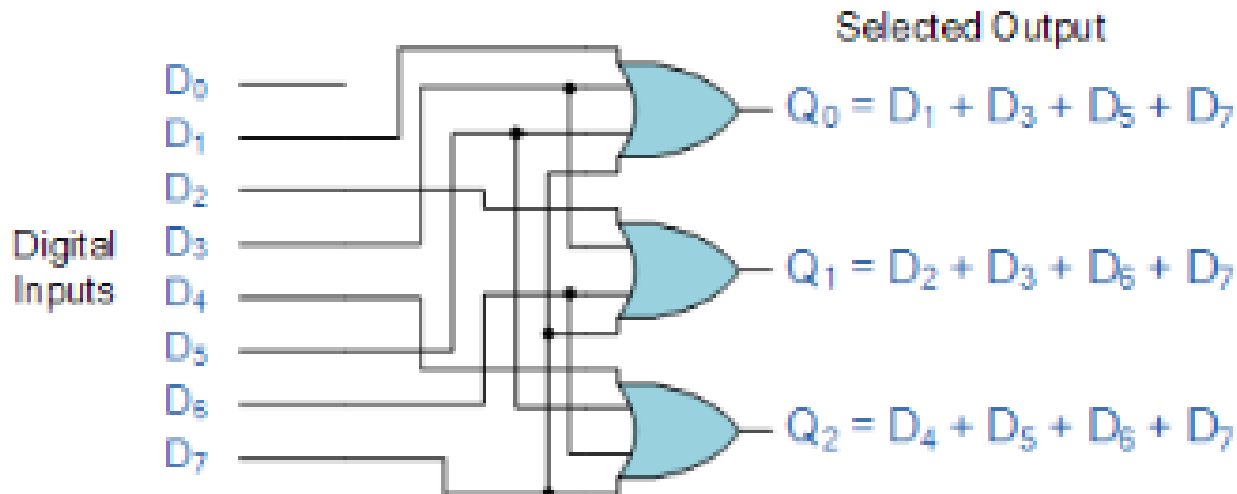These zero inputs would be ignored allowing the implementation of the final Boolean expression for the outputs of the 8-to-3 priority encoder.



8-to-3 Bit Priority Encoder in other modeling

```
// Priority encoder
module encode (A, valid, Y);
input  [7:0] A;                // 8-bit input vector
output [2:0] Y;                // 3-bit encoded output
output valid;                  // Asserted when an input is not all 0's
reg      [2:0] Y;              // target of assignment
reg      valid;

always @(A) begin
    valid = 1;
    casex (A)
        8'bXXXXXXXX1: Y = 0;
        8'bXXXXXXXX10: Y = 1;
        8'bXXXXXX100: Y = 2;
        8'bXXXXX1000: Y = 3;
        8'bXXX10000: Y = 4;
        8'bXX100000: Y = 5;
        8'bX1000000: Y = 6;
        8'b10000000: Y = 7;
        default: begin
            valid = 0;
            Y = 3'bX; // Don't care when input is all 0's
        end
    endcase
end
endmodule
```


Priority Encoder using if -else

```
Module
pri_encoder ( a, i,
en );
output reg [2:0] a ;
input en ;
input [7:0] i ;

always @ (en or i)
begin
    a = 0;
    if (en) begin
        if (i[1] == 1)
            a = 1;
        else if (i[2] == 1)
            a = 2;
        else if (i[3] == 1)
            a = 3;
```

```
    else if (i[4] == 1)
        a = 4;
    else if (i[5] == 1)
        a = 5;
    else if (i[6] == 1)
        a = 6;
    else if (i[7] == 1)
        a = 7;
    end
end
endmodule
```

8-to-3 Bit Priority Encoder in yet another modeling

```
1  module p_encoder (D, Q);
2      input [7:0] D;
3      output [2:0] Q;
4
5      assign Q = (D[7]==1) ? 3'b111:
6                  (D[6]==1) ? 3'b110:
7                  (D[5]==1) ? 3'b101:
8                  (D[4]==1) ? 3'b100:
9                  (D[3]==1) ? 3'b011:
10                 (D[2]==1) ? 3'b010:
11                 (D[1]==1) ? 3'b001:
12                 (D[0]==1) ? 3'b000;
13  endmodule
```

This modeling uses conditional operator.

(_____) ? A : C

You can do using “if, else”, too.


Revision of Verilog: if-else Statements

if statements allows the tool to decide, **depending on the conditions specified**, a statement is to be executed or not.

```
if( condition )  
    statement;
```

```
if( reset )  
    counter = 0;  
else  
    counter = counter + 1;
```

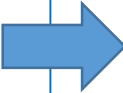If there are more than one statements within an if block, we can combine them using **begin -- end**. We can also **nest if-else** statements as in these examples



```
if( reset )  
begin  
    counter <= 0;  
    over_flow <= 0;  
end  
else if ( counter == 15 )  
begin  
    counter <= 0;  
    over_flow <= 1;  
end  
else  
begin  
    counter <= counter + 1;  
    over_flow <= 0;  
end
```

Case statement

```
case (case_expression)
  case_item1 : case_item_statement1;
  case_item2 : begin
                case_item_statement2a;
                case_item_statement2b;
                case_item_statement2c;
              end
  case_item3 : case_item_statement3;
  default   : case_item_statement5;
endcase
```


Never forget
Default !

Example

```
case (SEL2bit)
  00:SELO <= IN_A;
  01:SELO <= IN_B;
  default :
    SELO <= IN_C;
endcase
```

```
module MUX4 (A, S, F);
  input      [3:0] A;
  input      [1:0] S;
  output      F;
  reg        F;
  always @(A or S) begin
    case S
      2'b00 : F = A [0];
      2'b01 : F = A [1];
      2'b10 : F = A [2];
      default : F = A [3];
    endcase
  end
endmodule
```

Compare !

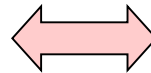

```
module MUX4 (A, S, F);
  input      [3:0] A;
  input      [1:0] S;
  output      F;
  reg        F;
  always @(A or S) begin
    if (S == 2'b00)
      F = A [0];
    else if (S == 2'b01)
      F = A [1];
    else if (S == 2'b10)
      F = A [2];
    else
      F = A [3];
  end
endmodule
```

Case statement

If statement

for - loop

The **<init>** code is executed once.



The **<test>** code returns a true/false and is tested before each iteration.

The **<body>** and **<end>** codes are executed each iteration.

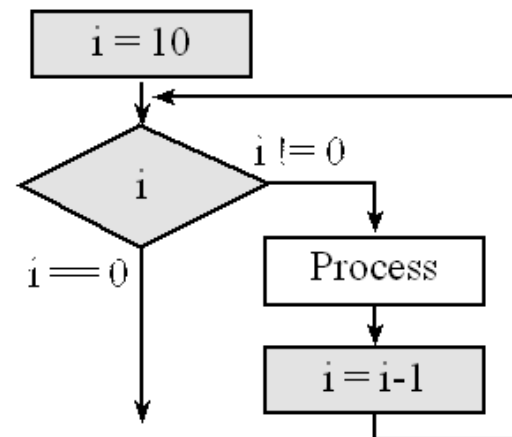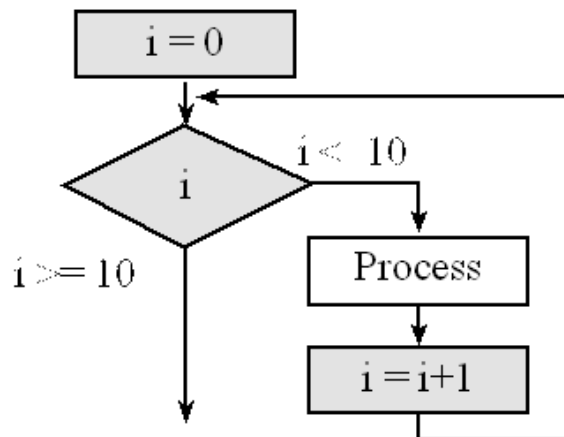example

```
for (i = 0 ; i < 4 ; i = i + 1)begin  
  DATA_B[i] = DATA_A[i];  
end
```

```
for(<init>; <test>; <end>)  
  <body>;
```



Procedural assignment

`begin ~ end`


```
always @( posedge CK or posedge RES ) begin
    if ( RES==1'b1 ) begin
        a_reg <= 1'b0;
        b_reg <= 1'b0;
    end
    else if ( ENBL==1'b1 ) begin
        a_reg <= a_in;
        b_reg <= b_in;
    end
end
```

Processed in the order of statements in code.

Blocking and non-blocking assignments


Blocking (operation Similar to S/W)
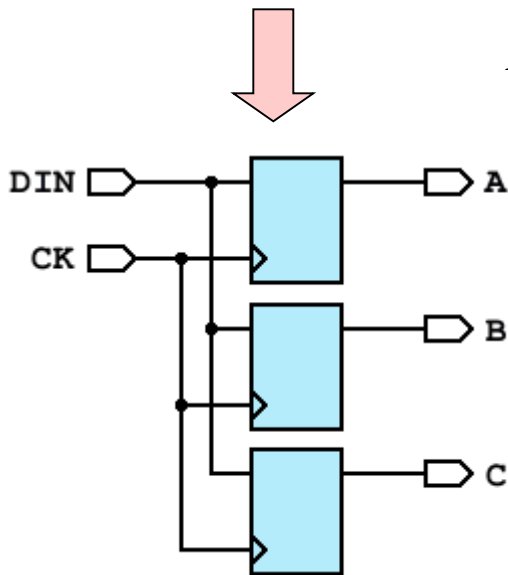
```
always @( posedge CK )  
begin  
    A = DIN;  
    B = A;  
    C = B;  
end
```



Non-blocking
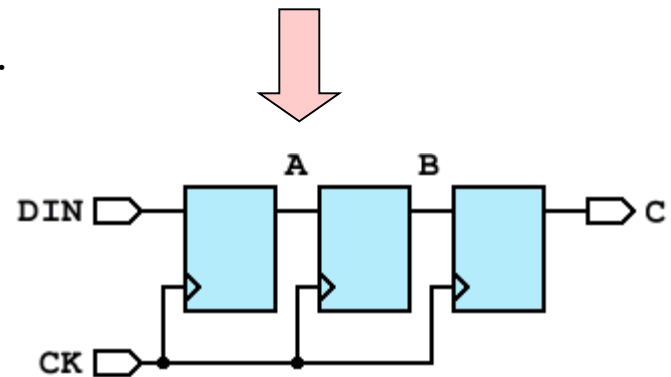
```
always @( posedge CK )  
begin  
    A <= DIN;  
    B <= A;  
    C <= B;  
end
```




After compilation...

Strongly recommend using **<=** instead of **=**.

Assignment statement: simple combinational logic

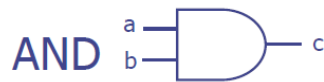
- continuously operating (according to the change of inputs) logic
- for wire type signals only → do not keep the value



```
//AND
module test(a,b,c);
input a,b;
output c;
```

```
assign c = a & b;
```

```
endmodule
```

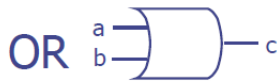

```
//OR
module test(a,b,c);
input a,b;
output c;
```

```
assign c = a | b;
```

```
endmodule
```

//Test回路

```
module test(A,B,C,D,E,F);
input A,B;
output C,D,E,F;
```


```
assign C = ~A & ~B;
```

```
assign D = ~A & B;
```

```
assign E = A & ~B;
```

```
assign F = A & B;
```

```
endmodule
```

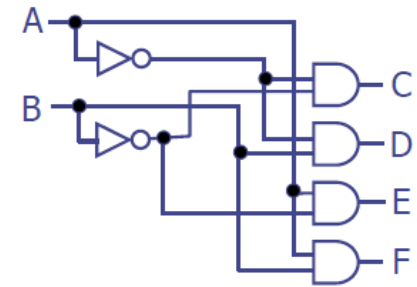


A	B	C	D	E	F
L	L	H	L	L	L
L	H	L	H	L	L
H	L	L	L	H	L
H	H	L	L	L	H

function statement: for more complicated combinational logic

if statements and case statements can be used.

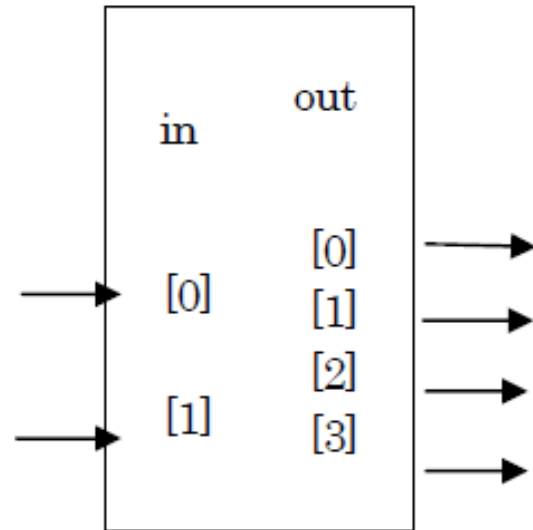example: 2 to 4 decoder

```
module dec2to4 ( in, out ) ;  
    input [1:0] in ;  
    output [3:0] out ;  
    function [3:0] dec;  
    input [1:0] in;  
    begin  
        case ( in )  
            0: dec = 4'b0001;  
            1: dec = 4'b0010;  
            2: dec = 4'b0100;  
            3: dec = 4'b1000;  
        endcase  
    end  
    endfunction  
    assign out = dec ( in ) ;  
endmodule
```



always statement: for sequential circuit

- Sequential logic triggered by clock, reset,, uses always statement, for repeated operations in particular.
- In always blocks, reg are used. Assignment to wire is a grammatical error.
- Assignment to reg should use **<=** . (= is likely to lead to mistakes.)

```
//加算演算子による4ビット・カウンタ
module counter(CLK,RESET,Q);
input CLK,RESET;
output [3:0] Q;
reg [3:0] Q;
always @ (posedge CLK or posedge RESET) begin
    if (RESET==1'b1)
        Q <= 4'h0;
    else
        Q <= Q + 4'h1;
    end
endmodule
```

always @ (event) :

posedge:

At the rising edge of CLK or RESET,
"begin – end" is executed always. !

negedge for falling edge